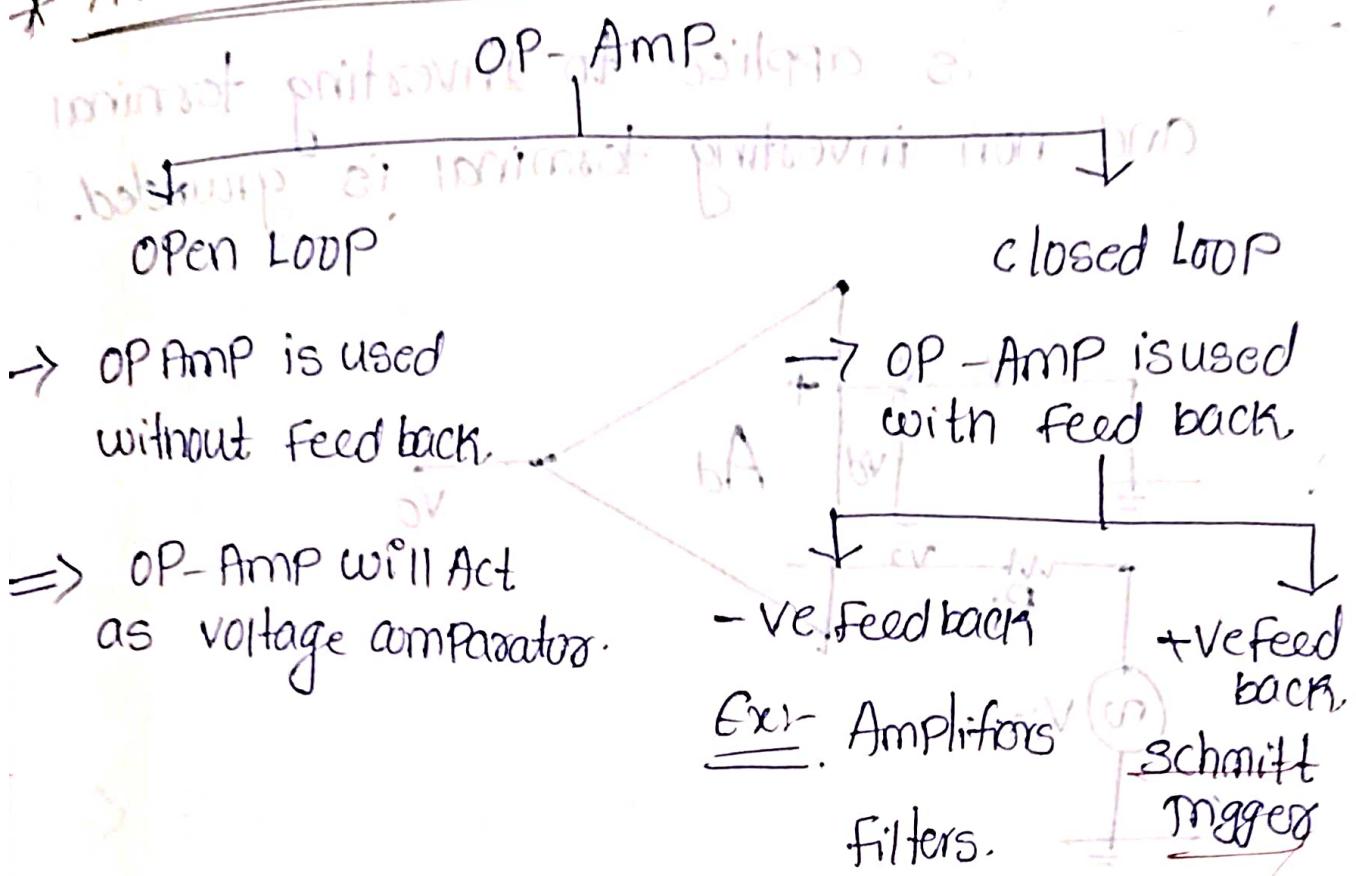


* Application of OP-Amp



* Open Loop OPAMP Configurations

⇒ Open Loop:- No connection (direct or indirect) exists between Input and Output.

→ Under open Loop, OP-Amp acts as high gain amplifier.

→ There are 3 open Loop configurations.

→ Inverting Amplifier


→ Non Inverting Amplifier

→ Differential Amplifier.

* Inverting amplifiers:-

⇒ Input is applied to Inverting terminal and non inverting terminal is grounded.

→ Input terminals

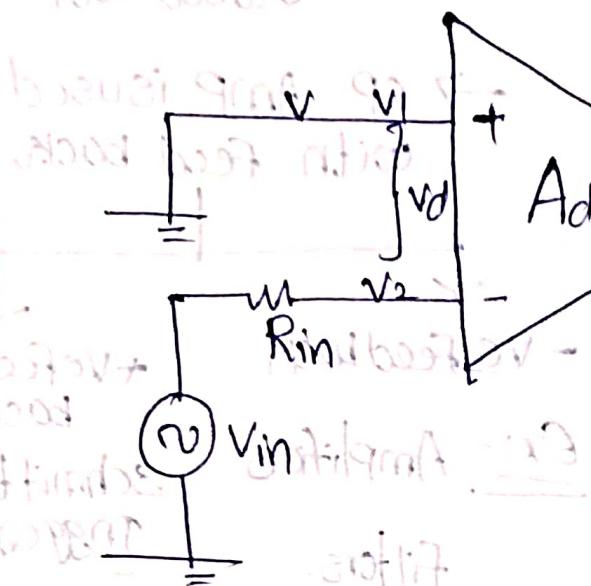

$$\Rightarrow V_1 = 0, \quad V_2 = V_{in}$$

⇒ The OIP & iIP relation of Inverting Amp

$$V_o = -Ad V_d = Ad(V_1 - V_2)$$

$$V_o = -Ad(0 - V_{in})$$


$$\boxed{V_o = -Ad V_{in}}$$

- sign indicates 180° Phase shift between input and output.

⇒ Here we are giving +ve voltage input and we will get -ve voltage as output & vice-versa.

* Non-Inverting Amplifiers:-

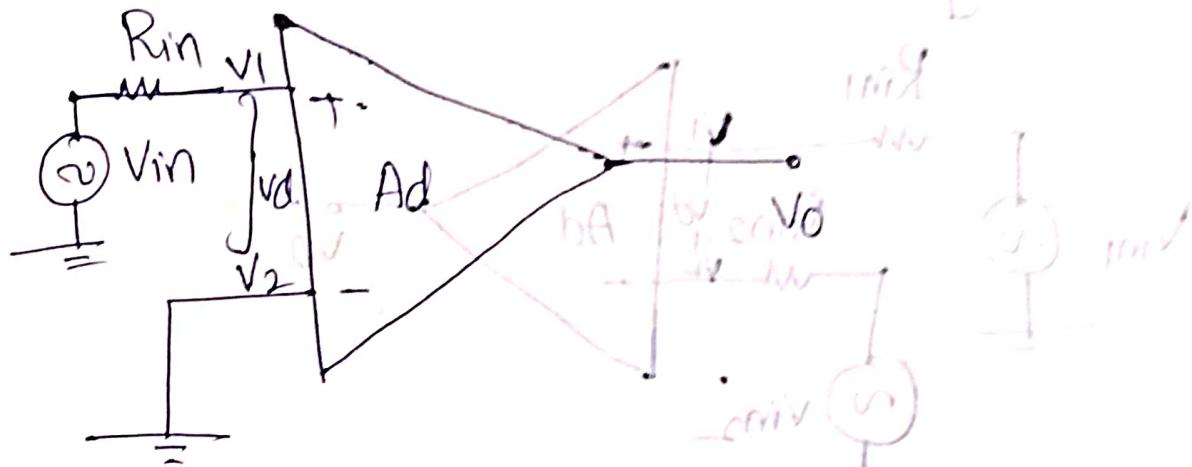\Rightarrow Input voltage is applied to non-inverting terminal and inverting terminal is grounded.



\Rightarrow Here $V_1 = V_{in}$, $V_2 = 0$.

\Rightarrow The OIP and IIP relation of Non-Inverting Amplifiers is given as $V_o = Ad(V_1 - V_2)$

$$V_o = Ad \cdot V_d = Ad(V_1 - V_2)$$

$$\boxed{V_o = Ad[V_{in}, V_2 = 0]}$$

$$\boxed{V_o = Ad[V_{in}]}$$

$$\boxed{V_o = Ad V_{in}}$$


\Rightarrow No phase shift between input and out.

Put-

Op-amp forward voltage gain is 10^6 .
Assume $V_o = 10^6 V_{in}$

* Differential Amplifier:-

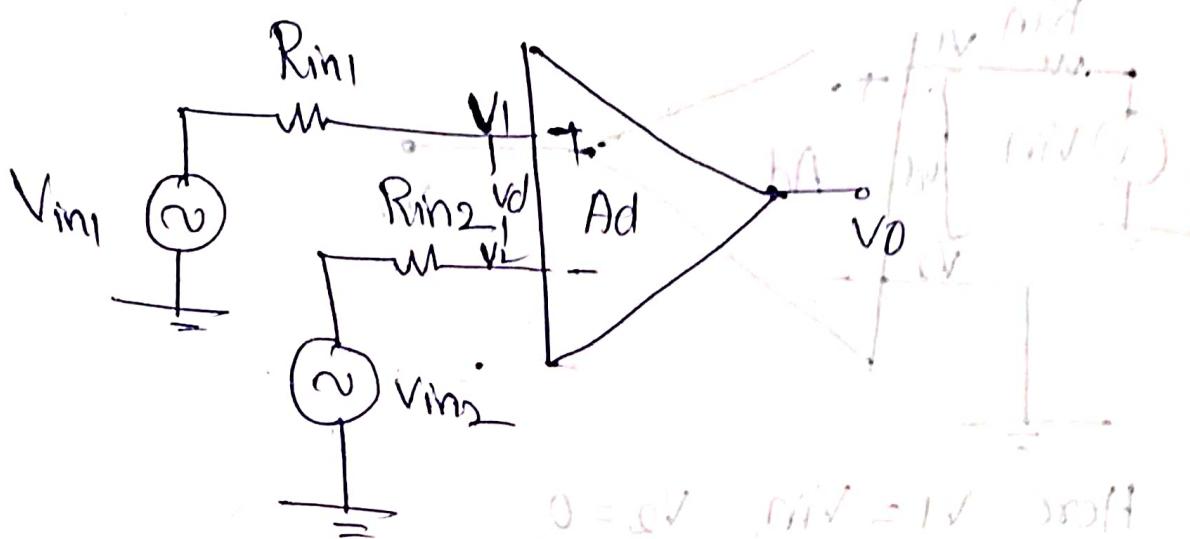- * Input is applied to both the terminals.
- * Amplifies the differences of two input signals.



\Rightarrow Here $V_1 = V_{in1}$, $V_2 = V_{in2}$

\Rightarrow The OIP & IIP relation of the diffamp

$$V_O = Ad \cdot V_d = Ad(V_{in1} - V_{in2}) = 0V$$

$$\boxed{V_O = Ad(V_{in1} - V_{in2})}$$

\Rightarrow Output Polarity depends on difference input Polarity.

\Rightarrow For Open Loop Configurations, mostly the output is $\pm V_{sat}$.


* Limitations

\Rightarrow only the smaller signals having low freq may be amplified.

- ⇒ open loop voltage gain varies with temperature and power supply.
- ⇒ bandwidth for open loop OP-Amp is negligibly small.
- ⇒ not suitable for linear applications.

* Closed Loop OP-Amp :-

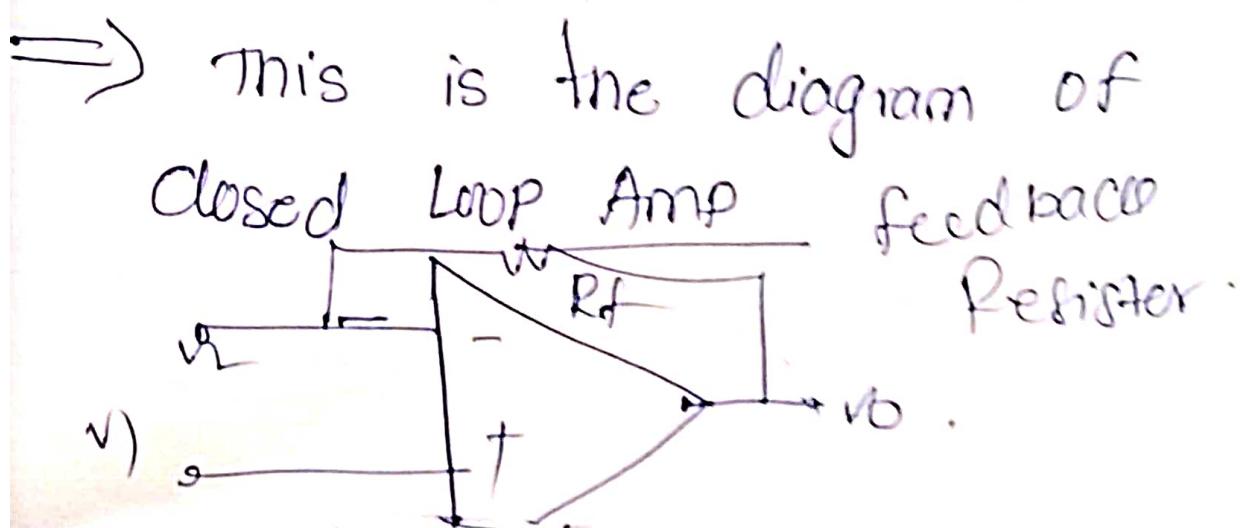- Feedback - A portion of the output signal is fed back to the input (is) called feedback.
- ⇒ Amplifiers using feedback are called closed loop amplifiers.
 - ⇒ The gain of the OP-Amp can be controlled, if feedback is introduced in the circuit.



Here from O/P to I/P Side we are giving
One Resistive feed back i.e. R_f .

Feedbacks

↓
Invertigating signal goes to output for C.

Positive feedback. → -ve feedback

⇒ If the I/P signal and feedback are in phase (0°) the feedback is called Positive feed back.

⇒ If the I/P signal & feedback sign are in out of phases (180°), The feedback is called Negative feedback.

* Most of the Linear Circuits use OP-Amp in a closed loop mode with -ve feedback with R_f


Advantages of negative feedback

- (1) It reduces the gain and makes it more controllable and more stable.
- (2) It reduces the possibility of distortion.
- (3) It increases the bandwidth of the system.
- (4) It increases the i/p resistance of O/P-PNP.
- (5) It decreases the o/p resistance of O/P-PNP.
- (6) It reduces the effect of temperature on the gain of the circuit.

$$\text{Given } V = 1V$$
$$\frac{10}{10+1} = \frac{10}{11} = 0.909$$
$$\frac{10}{10+1} = \frac{10}{11} = 0.909$$
$$0.909 \times 10A = 9.09A$$
$$\frac{9.09}{10} = 0.909$$
$$0.909 \times 10V = 9.09V$$


* Virtual Ground Concept :-

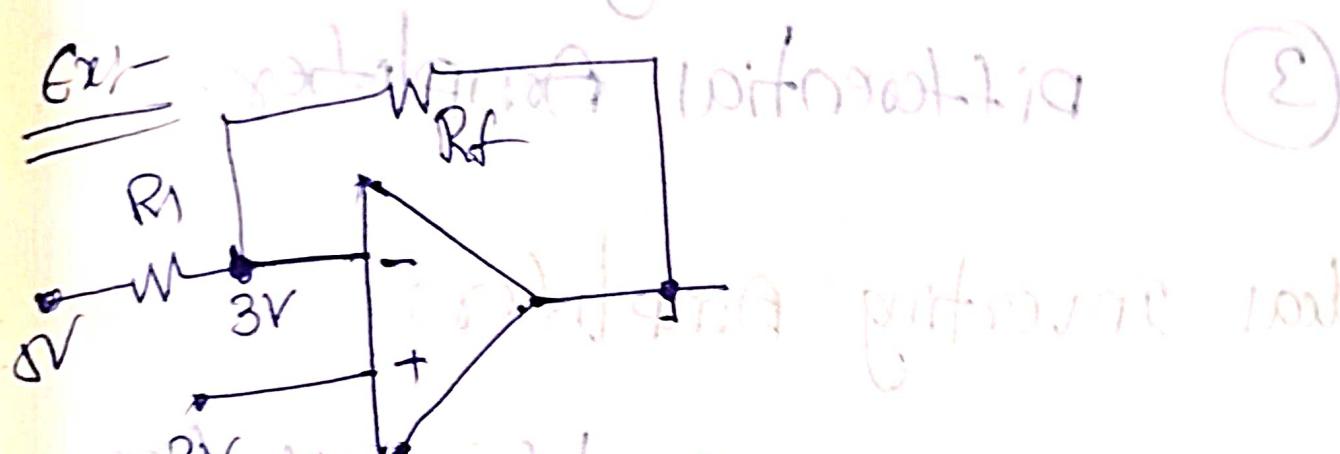* In OP-AMPS the term virtual ground means that net voltage at the particular node is almost equal to ground voltage (a)



* In the above circuit V_1 is connected to ground so $V_1 = 0$, thus V_2 also will be at ground potential as $0 = \text{ref. to ground}$

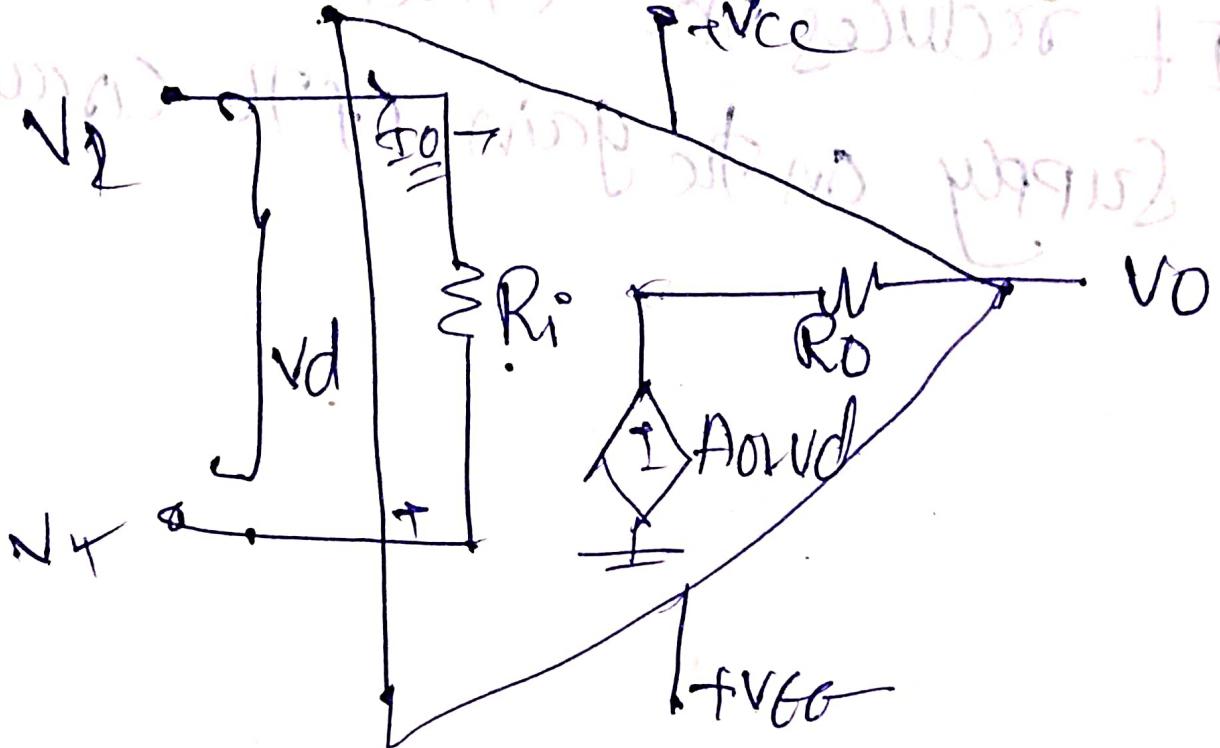\Rightarrow Consider the Equivalent Circuit of OP-AMP.



$$V_0 = \frac{AOL}{R_i} \cdot V_d$$

①

$$\underline{R_i = \infty}, \quad \underline{AOL = \infty}$$

$$V_{d1} = \frac{V_0}{\infty} \approx 0$$

$$V_1 - V_2 = 0$$

$$\boxed{V_1 = V_2}$$

$$\boxed{V_1 = V_L}$$

NOTE:-

* following Assumptions are used in analysis of -ve feed back OP-Amp Circuit.

- ① Inverting & non-inverting terminals are virtually shorted.
- ② Input currents of OP-Amp are negligible.

* Closed Loop OP-Amp Configurations

* In general OP-Amp is used in closed loop configuration to increase the linear range of operation.

→ Closed Loop OP-Amp can be configured into 3 types.

- ① Inverting Amplifier
- ② Non-Inverting Amp
- ③ Differential Amplifier


* Ideal Inverting Amplifier:

Ideal Inverting Amplifier: ~~Circuit diagram~~

As shown in fig.

⇒ Ideal means There is no loss.

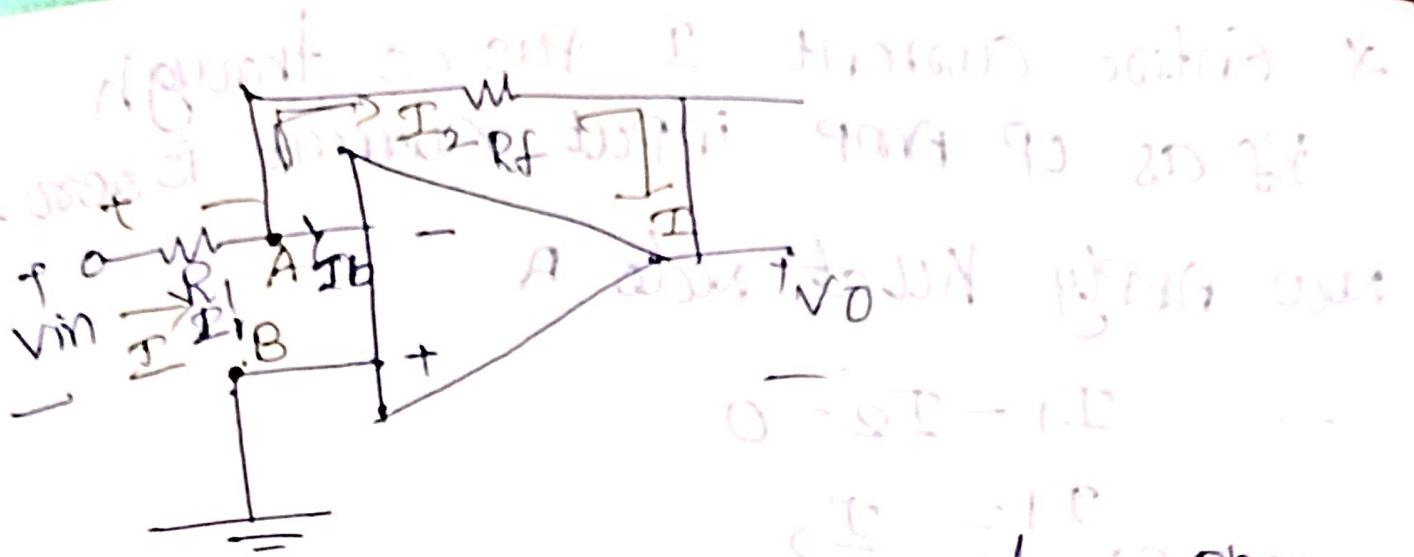In this ideal OP-Amp gain = $\frac{V_o}{V_i} = \infty$
Output Res ≈ 0 .



* An Amplifier which provides a phase shift of 180° between input and output is called inverting Amplifier.

* Derivation of closed-loop gain—

∴ According to $\frac{V_A}{V_{IN}} = -AV_L$.

$$\underline{V_A = V_B = 0}$$

~~At the iIP side. side~~

$$I_1 = \frac{V_{IN} - V_A}{R_1}$$

$$I_1 = \frac{V_{IN}}{R_1} \quad \text{--- } \textcircled{1}$$

From the out side

$$I_2 = \frac{V_A - V_O}{R_f} = -\frac{V_O}{R_f} \quad \text{--- } \textcircled{2}$$

* Entire current I passes through R_f as OP-AMP input current is 8 mA

Now apply KCL at node A

$$I_1 - I_2 = 0$$



$$I_1 = I_2$$

$C_2(0)$

$$\frac{V_m}{R_i} = \frac{-V_o}{R_f}$$


$$\frac{V_o}{V_m} = -\frac{R_f}{R_i}$$

$$\boxed{A_v = -\frac{R_f}{R_i}}$$

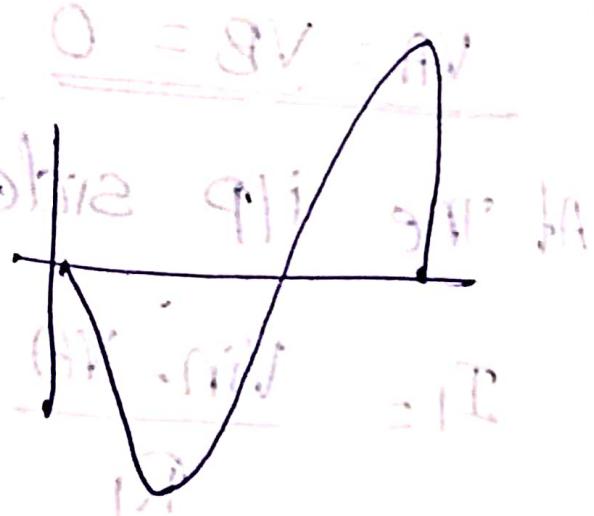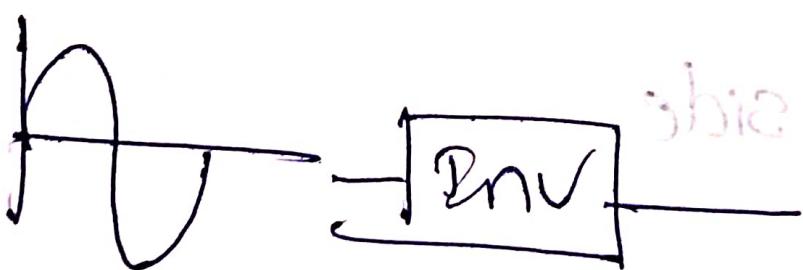

* Ideal Non-Inverting Amplifier

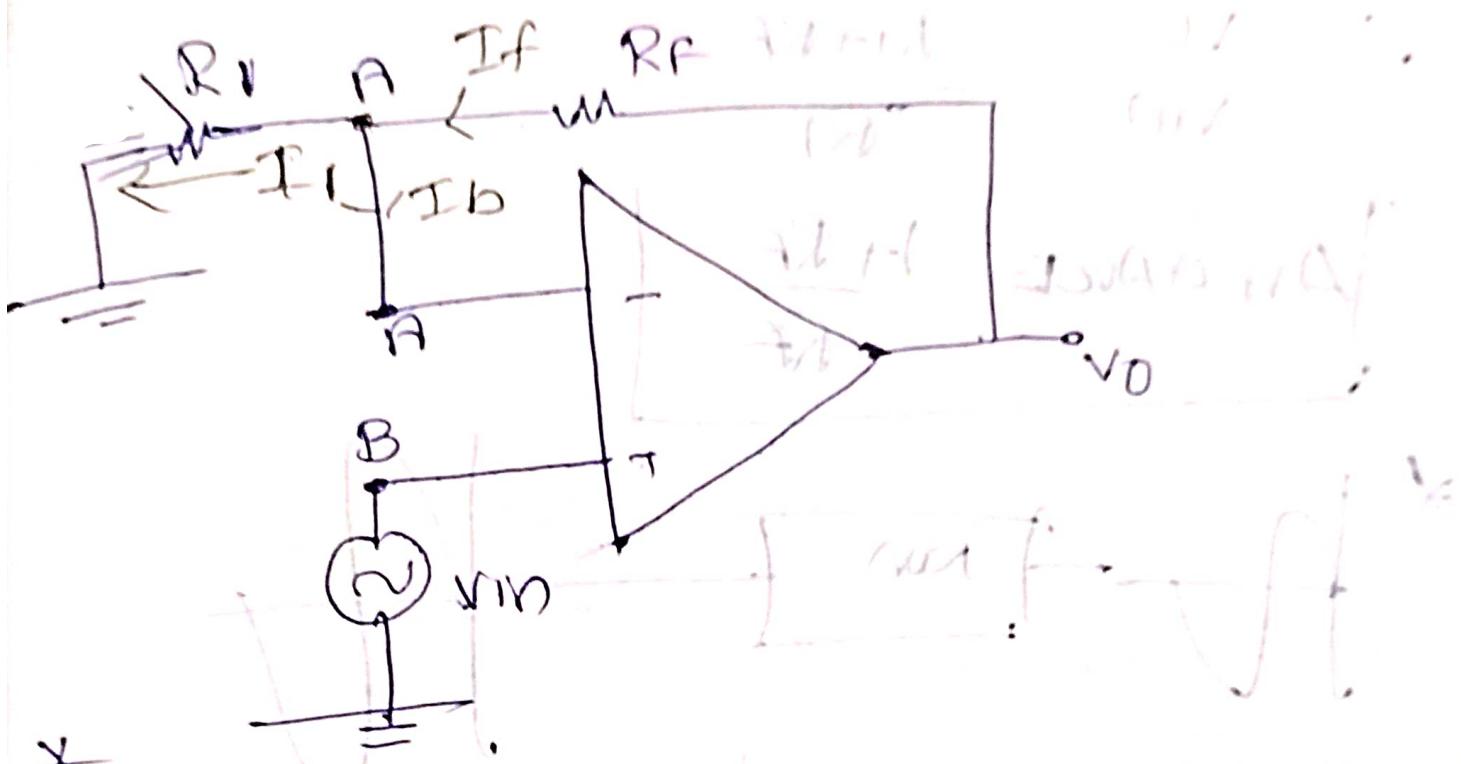An Amplifier which Amplifies the Input without producing any Phase shift between input and output is called Non-Inverting Amp



$$\therefore V_A = V_B = V_{IN}$$

$$\therefore I_1 = \frac{V_A - V_B}{R_1} = \frac{V_{IN}}{R_1} \quad (1)$$

$$\Rightarrow I_f = \frac{V_O - V_{IN}}{R_F} \quad (2)$$

now apply KCL at A $\omega > \omega_0$ (3)

$$I_f - I_1 - I_B = 0 \quad \omega > \omega_0 \quad (3)$$

$$\therefore I_1 = I_f \quad (4)$$


Equating eq (3) (4)

$$\frac{V_{IN}}{R_1} = \frac{V_O - V_{IN}}{R_A}$$

and then we get $V_O = V_{IN} \left(\frac{R_1 + R_F}{R_1} \right)$

$$\therefore \frac{V_O}{V_{IN}} = \frac{R_1 + R_F}{R_1}$$


~~AV FOR VCE = $\frac{1 + R_F}{R_F}$~~

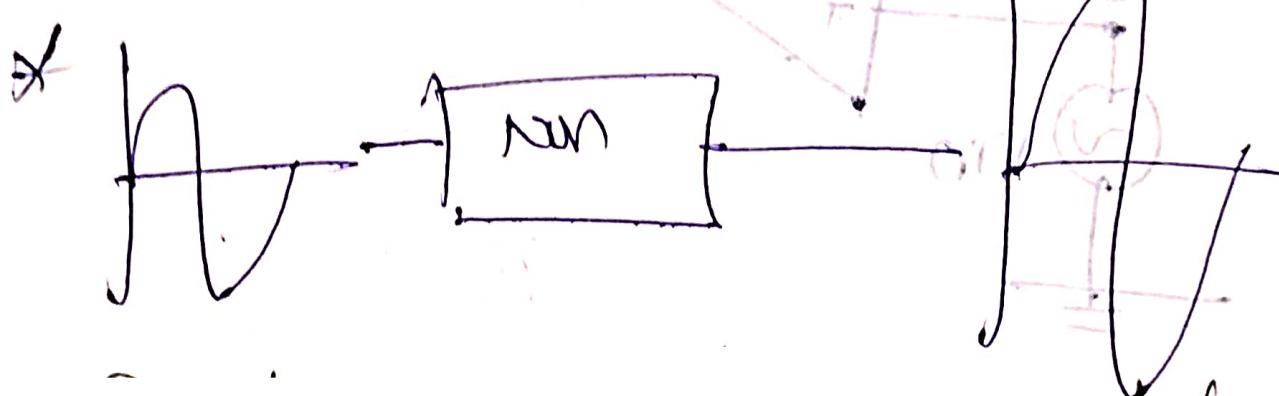

* OP-AMP as voltage follower:

A circuit in which the output voltage follows the input voltage is called voltage follower circuit.

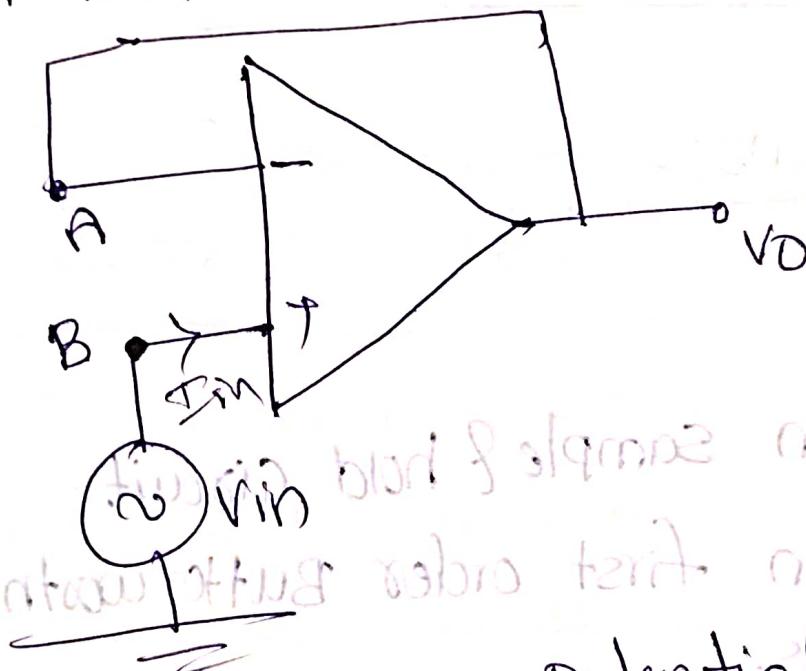⇒ The voltage follower circuit using OP-AMP is shown in fig



The node at B, potential $V_B = V_{in}$.
According $V_A = V_B$ $\therefore V_A = V_{in}$.


$$\therefore V_o = V_{in}$$

* I/P Resistance

hence

$$\frac{V_o}{V_{in}} = 1$$
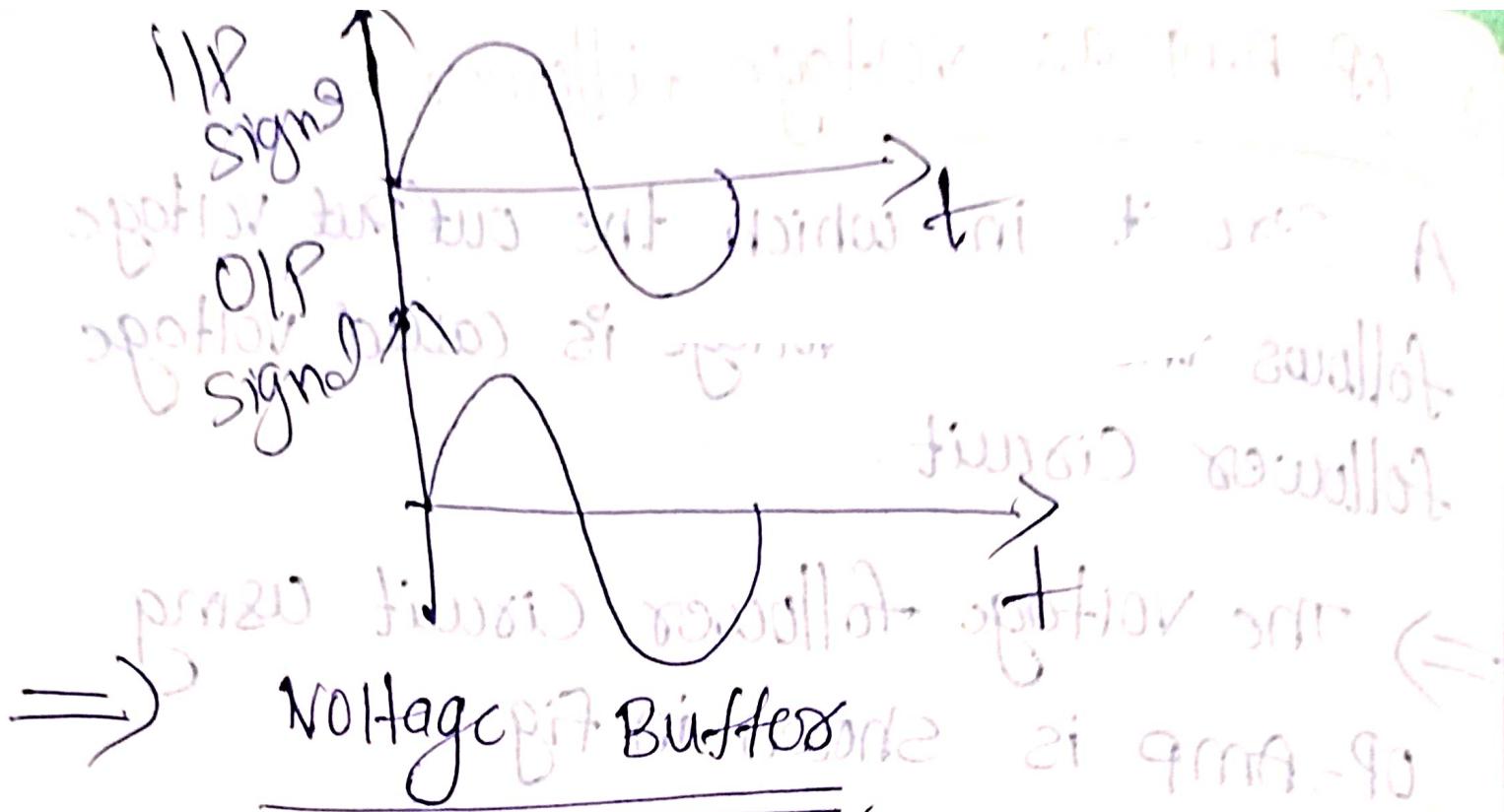
$$\frac{V_{in}}{I_{in}} = \frac{V_{in}}{0} = \infty$$



* Applications:-

- ① use in sample & hold circuit.
- ② use in first order Butterworth filters.
- ③ use in Instrumentation Amplifiers.

* Basic Applications of OP-Amp:-

- * OP-Amp is designed to do some mathematical operations such as
 - Addition (or) summing
 - Subtraction (or) differentiation
 - Multiplication
 - Integration
 - Comparison etc.

* Summer or Adder Circuit:-

⇒ As the input impedance of an OP-Amp is extremely large, more than one input signal can be applied to the inverting amplifier.

⇒ Such circuit gives the addition of the applied signals at the output.
Hence it is called Summer or Adder circuit.


⇒ Depending upon the sign of the output the summer circuits are classified as inverting summer and non-inverting summer.

$$\text{Summer} = \frac{\partial V}{\partial S_1} + \frac{\partial V}{\partial S_2} + \frac{\partial V}{\partial S_3}$$

* Inverting Summer:-

⇒ In this circuit, all the input signals to be added are applied to the inverting input terminal of the OP-AMP.

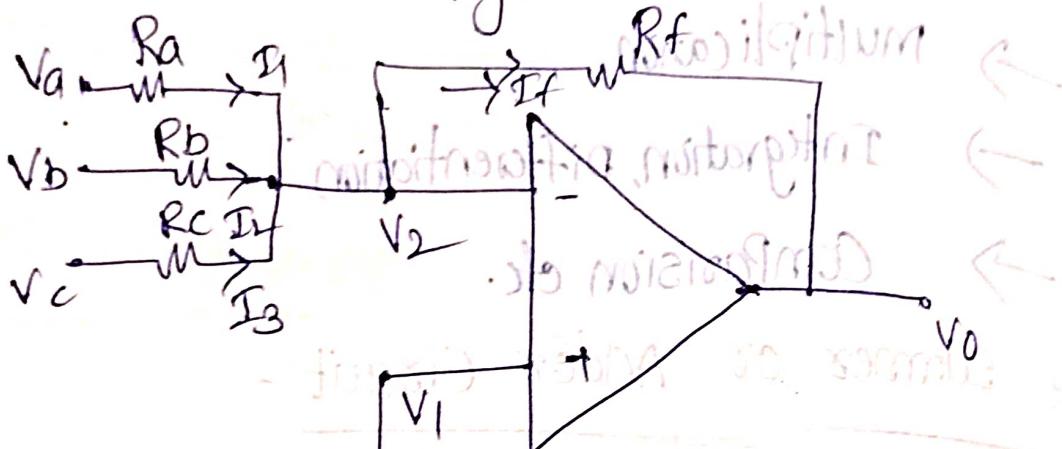⇒ The circuit with two input signals is shown in figure



Apply KCL at node V_2

$$I_1 + I_2 + I_3 - I_f = 0$$

$$I_1 + I_2 + I_3 = I_f$$

$$\frac{V_a - V_2}{R_a} + \frac{V_b - V_2}{R_b} + \frac{V_c - V_2}{R_c} = \frac{V_2 - V_o}{R_f}$$

Now that According to V_b , from $V_1 = V_2 = 0$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$

The Output Voltage

$$V_o = \frac{R_f}{R_1} [\frac{R_f}{R_1} V_a + \frac{R_f}{R_2} V_b + \frac{R_f}{R_3} V_c]$$

\Rightarrow If This Circuit shown $R_a = R_b = R_c = R$

$$V_o = -\frac{R_f}{R} [V_a + V_b + V_c]$$

\Rightarrow when $R_f = R$ then the output voltage is equal to negative sum of all inputs

$$V_o = -(V_a + V_b + V_c)$$

* Based on the values of R_f and R in the circuit, may be acts as scaling amplifier or average amplifier.

case 1. $\frac{R_f}{R_a} \neq \frac{R_f}{R_b} \neq \frac{R_f}{R_c}$

$$V_o = - \left(\frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c \right)$$


Case 2 $R_a = R_b = R_c = R$ & $\frac{R_f}{R} = 1/n$ where n is the number of IP then $R_f/R = 1/n$

$$V_o = - \frac{(V_a + V_b + V_c)}{3}$$
 (average amp)

v

Non Inverting Adder:

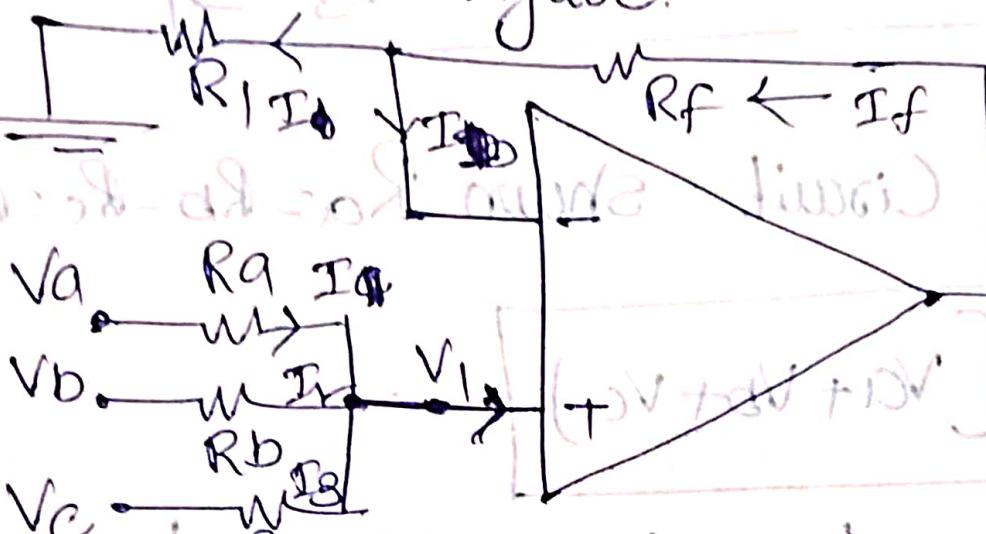Non Inverting Adder Circuit As Shown in Figure.



\Rightarrow now we want to calculate output voltage V_0 .

\Rightarrow Apply KCL at node V_1

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_a - V_1}{R_a} + \frac{V_b - V_1}{R_b} + \frac{V_c - V_1}{R_c} = 0$$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = V_1 \left[\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c} \right]$$

$$V_i = \frac{V_a + V_b + V_c}{\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c}}$$

Eq ①

\Rightarrow If we know that the output equation for non-inverting Amplifiers

$$V_o = \left(1 + \frac{R_f}{R_1}\right) \cdot V_i$$

\therefore sub Eq ① in Eq ②

$$V_o = \left(1 + \frac{R_f}{R_1}\right) \left[\frac{V_a + V_b + V_c}{\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c}} \right]$$

$$\text{Let AS taken } R_a = R_b = R_c = R = \frac{R_f}{2}$$

$$V_o = \left[1 + \frac{2R}{R}\right] \left[\frac{V_a + V_b + V_c}{R} \right]$$

$$3/ \frac{V_a + V_b + V_c}{R} \cdot \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$

B/R

\therefore The output voltage


$$V_o = (V_a + V_b + V_c)$$

\therefore The output voltage is sum of input voltages.

* Subtractor (or) Difference Amplifier

\Rightarrow Similar to the summer circuit, the subtraction of two input voltages is possible with help of OP-Amp circuit, called subtractor (or) difference amplifier circuit.

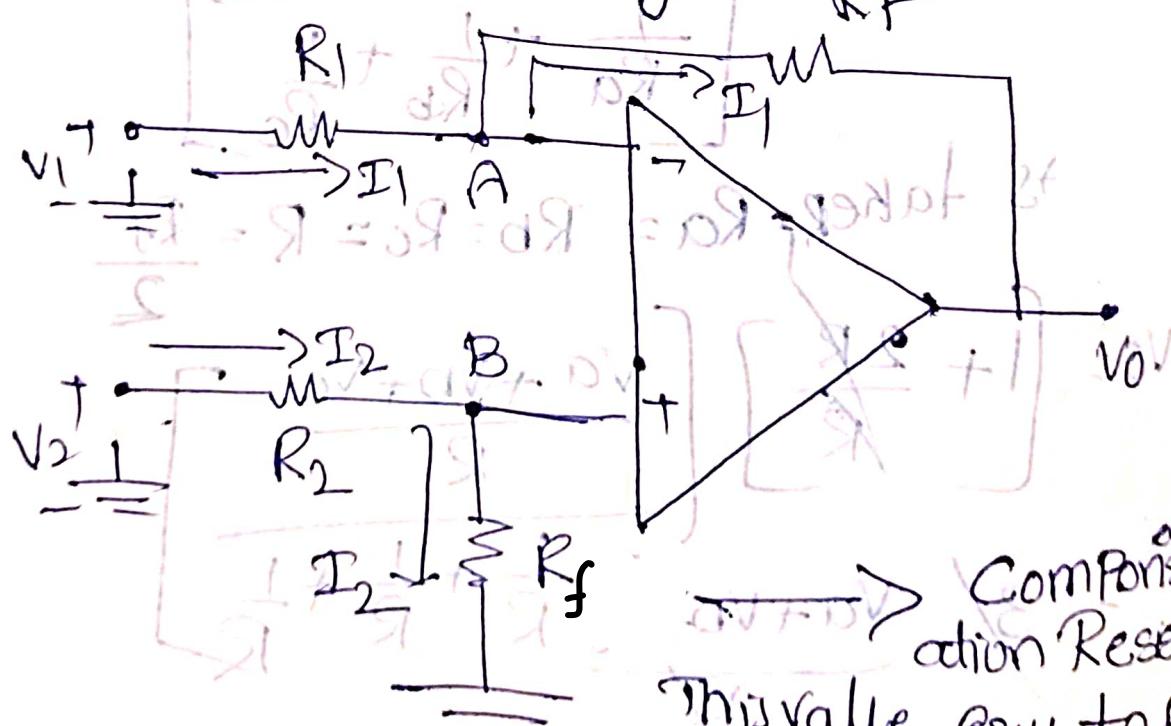\Rightarrow The circuit diagram of subtractor circuit as shown in figure.




\Rightarrow Compensation Resistor
This value equal to feed back Resistance.

- * calculation of V_{O1}
- * As we are having two inputs superposition theorem can be used to find the output voltage

$\Rightarrow V_{O1}$ - Output voltage when v_1 acting ($v_2=0$)
 V_{O2} - Output voltage when v_2 acting ($v_1=0$)

case1 v_1 Acting ($v_2=0$)

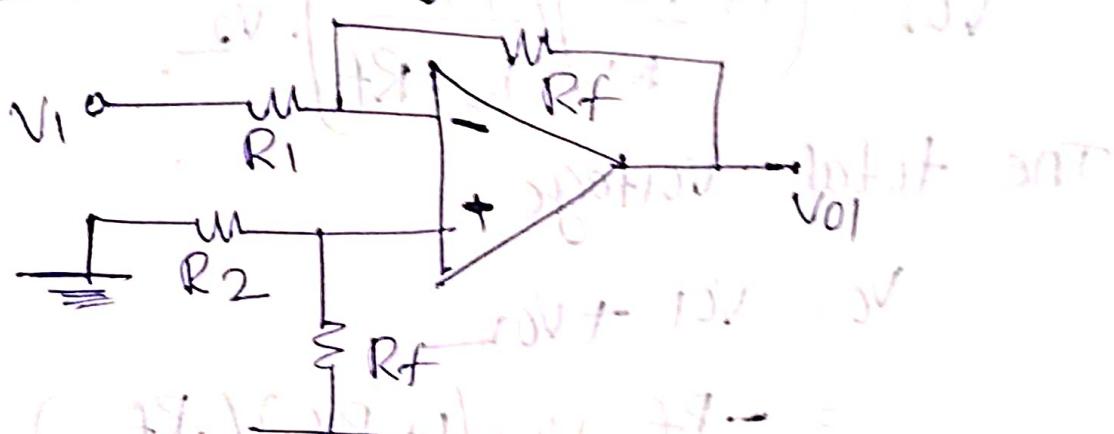


This circuit can act as Inverting Amplifier

$$\therefore V_{O1} = -\frac{R_f}{R_1 + 1} \cdot V_1 \quad \text{--- (1)}$$

Case2

v_2 Acting ($v_1=0$)

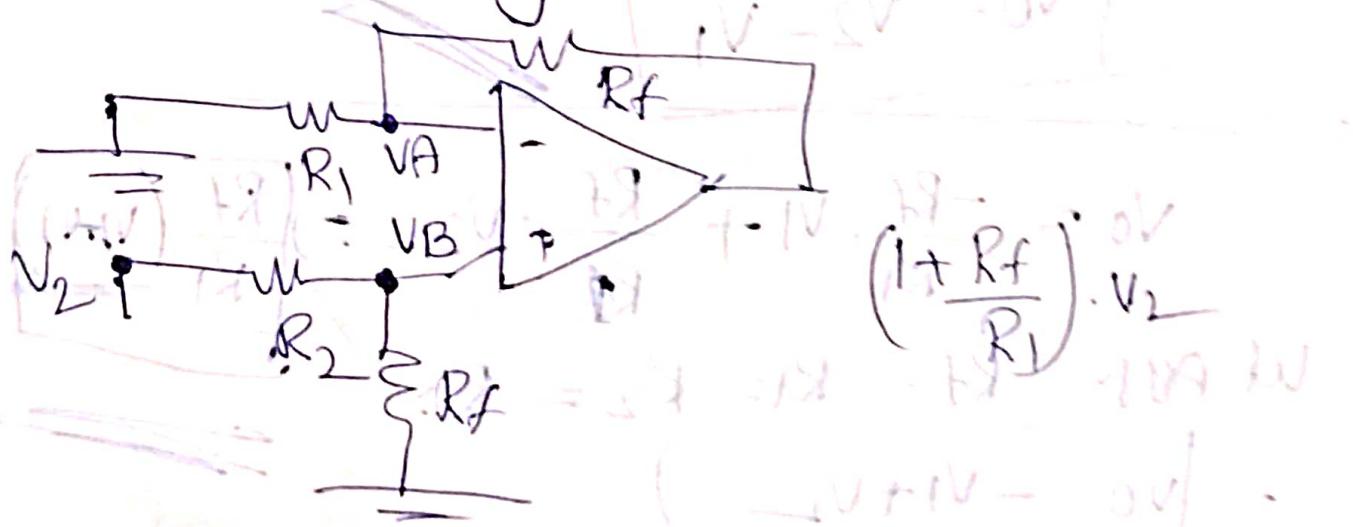

APPLY VOLTAGE DIVIDER Rule

Given value $V_B = \left(1 + \frac{R_f}{R_1}\right) \cdot V_{IN}$

∴ The output puts voltage $V_{OUT} = V_B - 10V$

$$V_{OUT} = \left(1 + \frac{R_f}{R_1}\right) \cdot V_B - 10V$$

$$V_{OUT} = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_f}{R_2 + R_f}\right) \cdot V_2$$

∴ The total voltage $V_O = V_{OUT}$

$$V_O = V_{IN} + \left(-\frac{R_f}{R_1} \cdot V_1 + \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_f}{R_2 + R_f}\right) V_2\right)$$

Assume $R_1 = R_2 = R$

$$V_O = \frac{R}{R + R} \cdot V_1 + \left(1 + \frac{R}{R}\right) \left(\frac{R}{R + R}\right) V_2$$

$$\therefore V_O = V_2 - V_1$$

$$V_O = -\frac{R_f}{R_1} \cdot V_1 + \frac{R_f}{R_1} \cdot V_2 \Rightarrow \frac{R_f}{R_1} (V_2 - V_1)$$

Let Assume $R_f = R_1 = R_2 = R$

$$\therefore V_O = -V_1 + V_2$$


$$\therefore [V_o = (V_2 - V_1)]$$

\Rightarrow output voltage is equal to the subtraction
of two input signals

* Logarithmic Amplifier

→ The fundamental log amplifier is formed by placing a diode or a transistor in the negative feedback path of the OP-AMP.

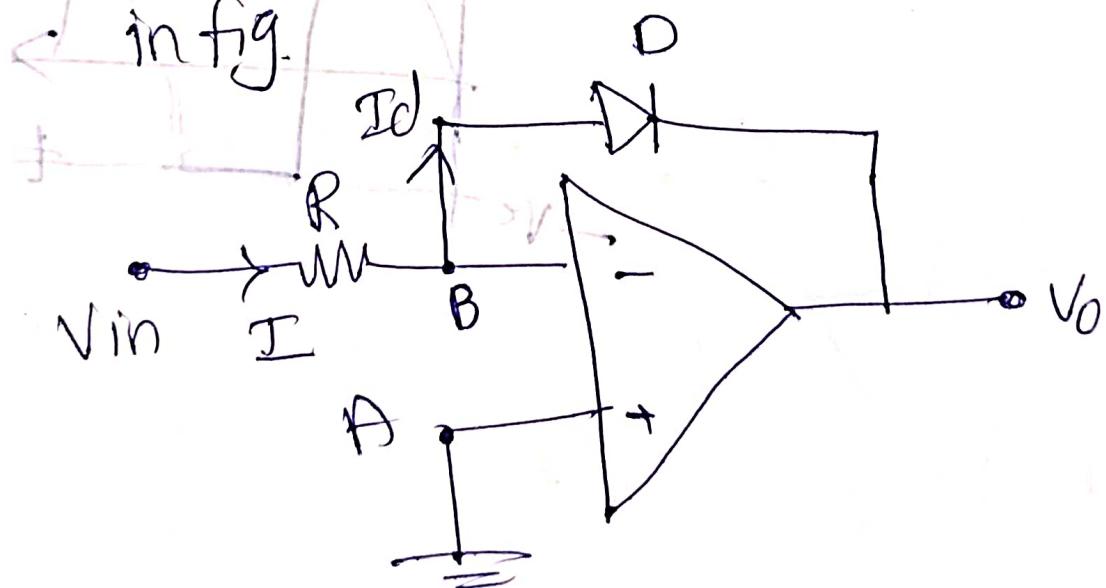⇒ The circuit diagram of basic log amplifier using diode is shown in fig.



⇒ The diode 'D' is used in the negative feedback path. The negative feedback path is grounded at node 'A'. ∴ The node 'B' is grounded. ∴ The node 'B' is at virtual


ground $V_B = 0$ (given)

$$\therefore I = \frac{V_{in} - V_B}{R} = \frac{V_{in}}{R} \rightarrow \text{Diode}$$

\Rightarrow As the OP-Amp input current is zero.

$$\therefore I = I_f = \text{Diode current}$$

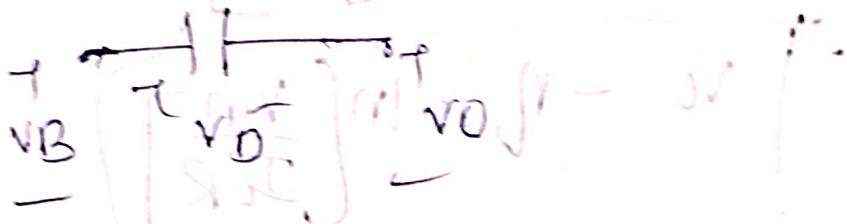now I_f is the current through diode and voltage across diode is $V_B - V_0$ ie $-V_0$



$$-V_B + V_D + V_0 = 0$$

$$V_0 = V_B + V_D = -V_0 \quad (V_B = 0)$$

$$\therefore V_0 = -V_0$$

We know that diode current

$$I_f = I_0 [e^{\frac{V_0}{nV_T}} - 1] \rightarrow \text{copy}$$

$$\therefore I_f = I_0 e^{\frac{V_0}{nV_T}} - I_0$$

$$I_f = I_0 e^{\frac{V_0}{nV_T}} \rightarrow \text{Q}$$

\therefore equating ① ②

$$\frac{V_{in}}{R} = I_0 e^{\frac{V_o}{nVT}}$$

$$\frac{8V - nV}{R} = I_0 \quad \therefore$$

$$\frac{V_{in}}{I_0 \cdot R} = e^{\frac{V_o}{nVT}}$$

$$\therefore \frac{V_o}{nVT} = \ln \left[\frac{V_{in}}{I_0 \cdot R} \right] = FC = T$$

$$V_o = nVT \ln \left[\frac{V_{in}}{I_0 \cdot R} \right]$$

$$V_o = -nVT \ln \left[\frac{V_{in}}{I_0 \cdot R} \right]$$

$$(0 = 8V) \quad V_o = -nVT \ln \left[\frac{V_{in}}{I_0 \cdot R} \right]$$


\Rightarrow Output voltage is a function of logarithm of the input voltage V_{in} .

Anti-log Amplifier

Anti-log Amplifier is an inverting Amplifier in which the input Resistor is replaced by a diode.

- The output is proportional to anti-log of input voltage.

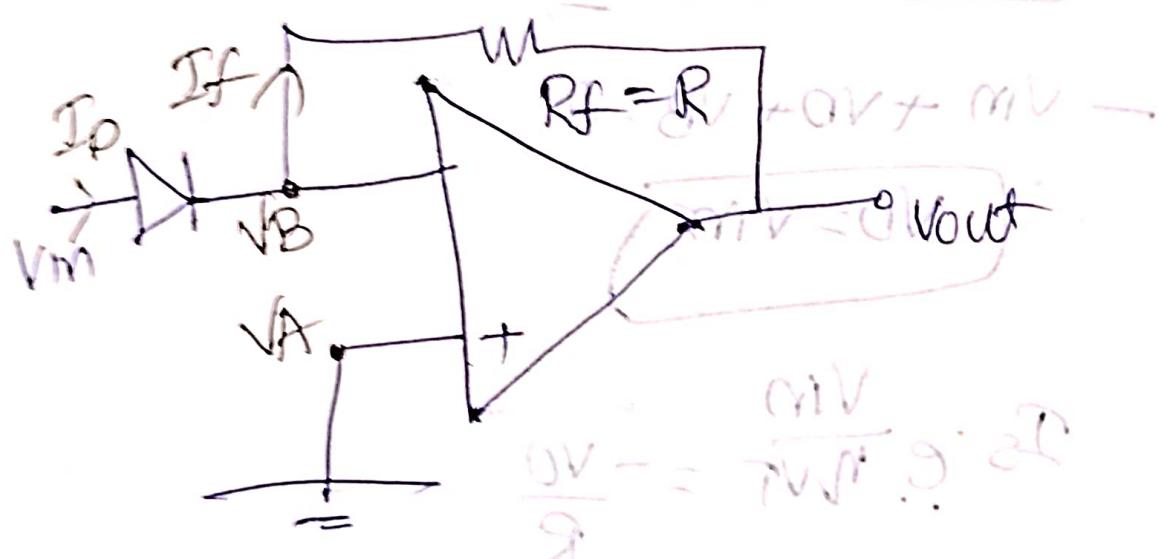The Ckt diagram of anti-log Amplifier is shown in fig.



Apply KCL at node B

$$I_o = I_f \quad \text{or} \quad I_o = I_s [e^{\frac{V_o}{nV_T}} - 1]$$

I_s = saturation current of diode

V_f = forward voltage of diode

V_t = Thermal Voltage

η = ideality factor value between 1 & 2

$$I_D = I_S e^{\frac{V_D}{\eta V_T}} \quad \text{for } V_D > 0$$

$V_D = V_B - V_0$

$$I_D = I_S e^{\frac{V_D}{\eta V_T}} = \frac{I_S}{R} e^{\frac{V_D}{\eta V_T}}$$

$$\therefore I_S e^{\frac{V_D}{\eta V_T}} = \frac{I_S}{R} e^{\frac{V_D}{\eta V_T}}$$

$$V_m + V_0 + V_B = 0$$

$$-V_m + V_0 + V_B = 0$$

$$V_0 = V_m$$

$$I_S e^{\frac{V_m}{\eta V_T}} = -\frac{V_0}{R}$$

Taking log on both sides

$$\log(V_0) = -I_S \cdot R \cdot \frac{1}{\eta V_T} \log e$$

$$= \left[\frac{1}{I_S \cdot R \cdot \eta V_T} \right] (V_m \log e)$$

$$V_0 = -I_S \cdot R \cdot \text{Antilog} \left(\frac{V_m}{\eta V_T} \right)$$

Considering I_S , η , V_T , R and I_S const.


$$\therefore V_0 \propto \text{Antilog} \left(\frac{V_m}{\eta V_T} \right) = e^V$$

Multiplex


In analog - signal processing the need often arises for a circuit that takes two analog input and produces an output proportional to their product. Such circuits are termed analog multipliers.

⇒ Analog multiplier is a circuit in which the output voltage is proportional to multiplication of input voltages.

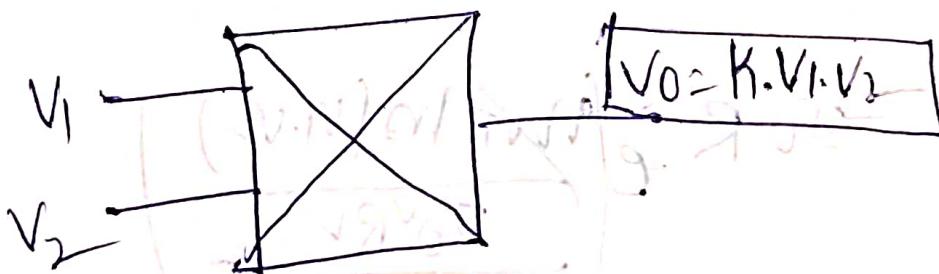∴ The symbol Repre of multiplier As shown in fig.



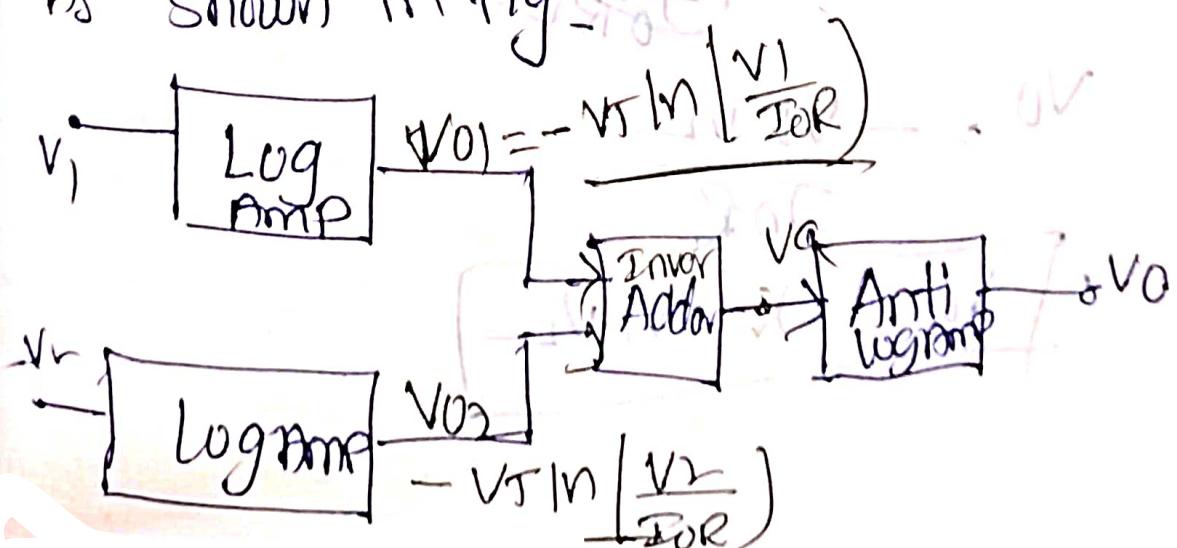The block diagram of multiplier can be shown in fig.



i) The output voltage of Inv

$$V_o = -I_{OR} R \ln \left(\frac{V_1}{V_2} \right)$$

Output voltage $V_o = I_{OR} R \ln \left(\frac{V_1}{V_2} \right)$

ii) The O/P of anti log Amp

$$V_o = -I_{OR} e^{\frac{V_1}{nVT}}$$

$$V_o = -I_{OR} e^{\frac{nVT \ln(V_1/V_2)}{I_{OR} R}}$$

$$V_o = -\frac{V_1 \cdot V_2}{I_{OR}}$$

$$V_o = -\frac{V_1 \cdot V_2}{I_{OR}}$$

$$\boxed{V_o = -\frac{V_1 \cdot V_2}{I_{OR}}}$$

* open Loop - OP-AMPS: -

* Comparators: -

A comparator is an electronic circuit, which compares the two inputs that are applied to it and produces an output. The output value of the comparator indicates which of the inputs is greater or lesser.

* Comparator is nothing but an Open Loop OP-AMP, with two inputs and one output.

* It compares a signal voltage applied to one input to OP-AMP with known voltage applied to other input. The output of comparator is either positive saturation or negative saturation, depending on which input is larger.


* It has following types.

① Inverting Comparator

② Non-Inverting Comparator

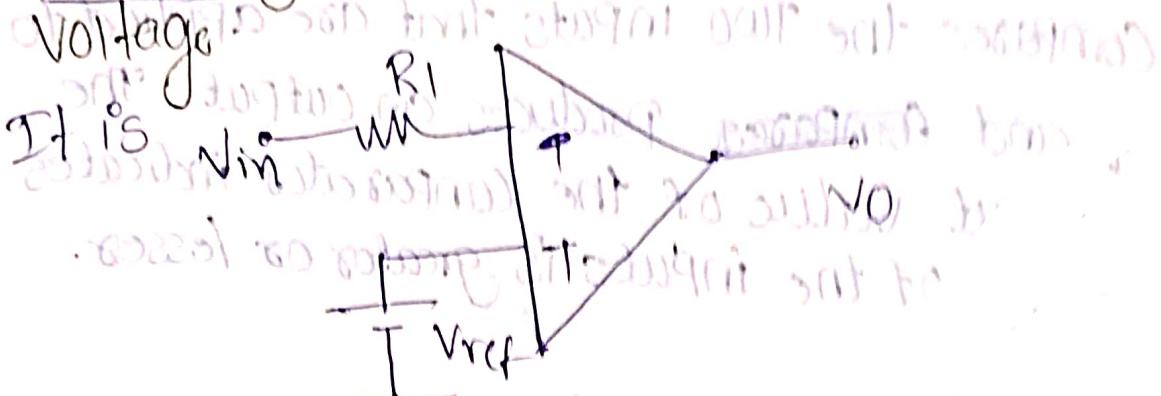(b) Inverting output in the


* Diverging Comparator with +ve Reference



* Operation


→ When V_{in} is less than V_{ref} , the voltage at non-inverting terminal is greater than voltage at inverting terminal. This makes differential voltage V_{id} positive and hence output will be in Positive Saturation ($+V_{sat}$).

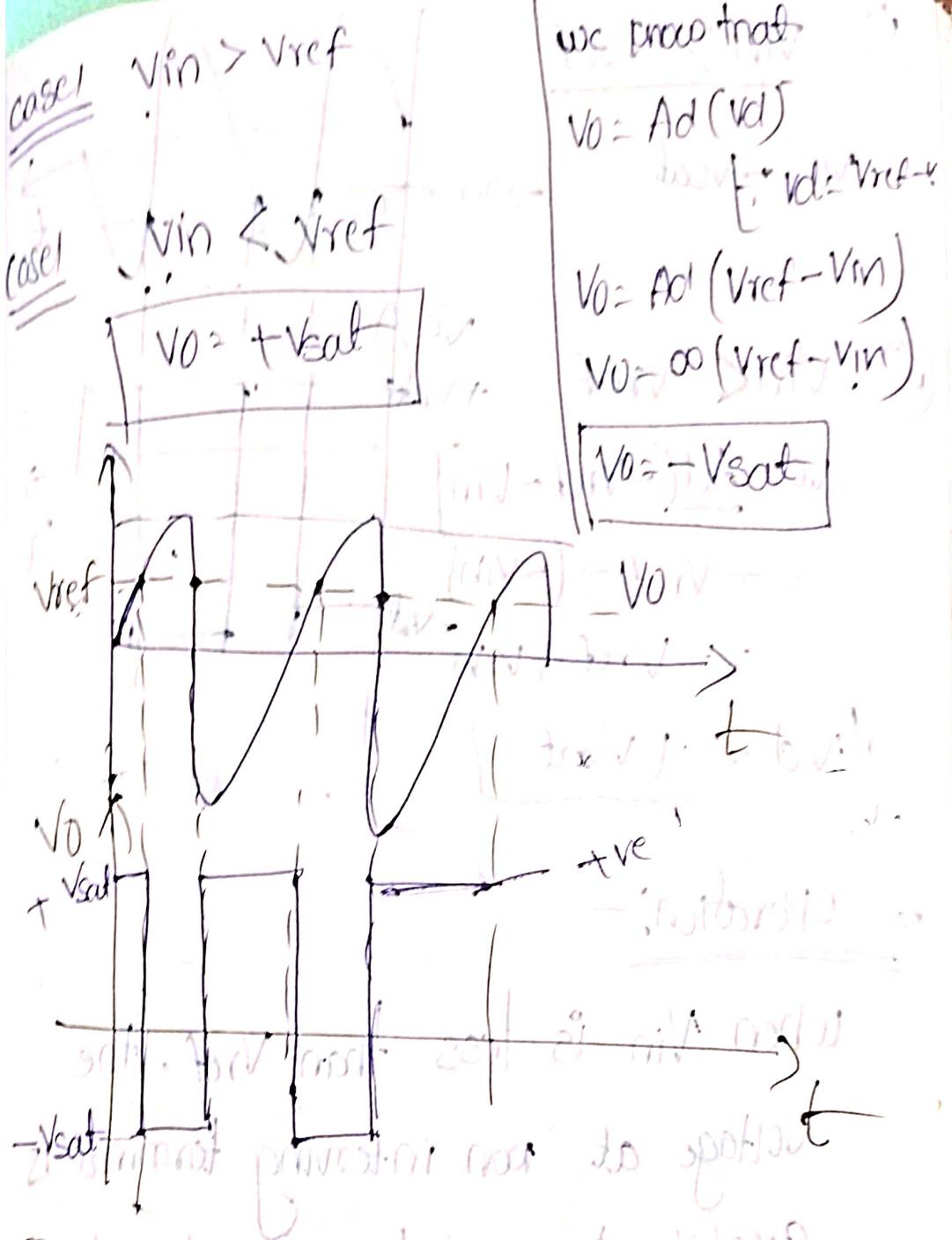→ When V_{in} is greater than V_{ref} , the voltage at inverting terminal is greater than voltage at non-inverting terminal. This makes differential voltage V_{id} negative and hence output will be in negative saturation ($-V_{sat}$).



① Inverting Comparator with -Ve Reference Voltage

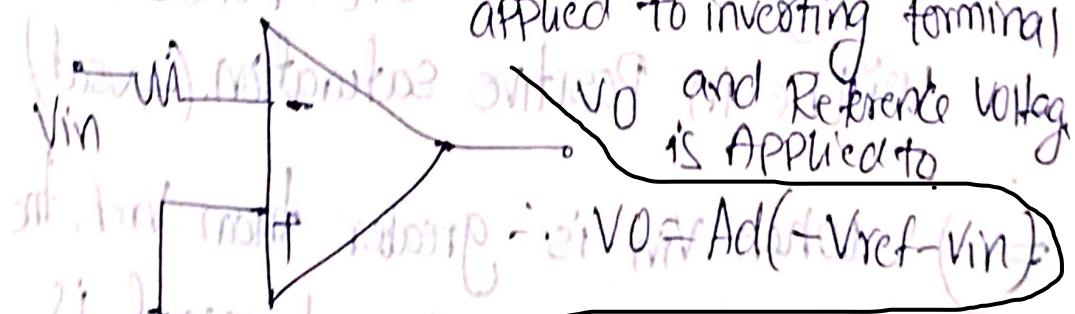* It is the comparator in which input is applied to inverting terminal



* Reference voltage applied is -ve

① Vin < Vref

$$mVd = Vsat - (-3)Vref$$

$$(mVd + Vsat) \approx Vsat$$

② Vin > Vref

$$\rightarrow mVd = -Vref(-Vref - Vin)$$

$$= -Vref - (-Vin)$$

$$\approx -Vref + Vin$$

$$\boxed{mVd = -t Vsat}$$

* Operation:-

when Vin is less than $Vref$, the voltage at non inverting terminal is greater than voltage at inverting terminal. This makes the differential input voltage Vd positive and hence output will be in positive saturation ($+Vsat$)

(+) when Vin is greater than $Vref$ the voltage at inverting terminal is greater than voltage at non-inverting terminal.

this makes the differential voltage V_{id} negative and hence output will be in negative saturation ($-V_{sat}$).
and in transient condition

* SCHMITT TRIGGER - (Regenerative feedback)


- The class of comparators which use the positive (Regenerative) feedback is known as the schmitt trigger or regenerative comparator.

⇒ It can be classified into 2 types.

- ① Inverting schmitt trigger
- ② Non-Inverting schmitt trigger.

* Inverting schmitt trigger-

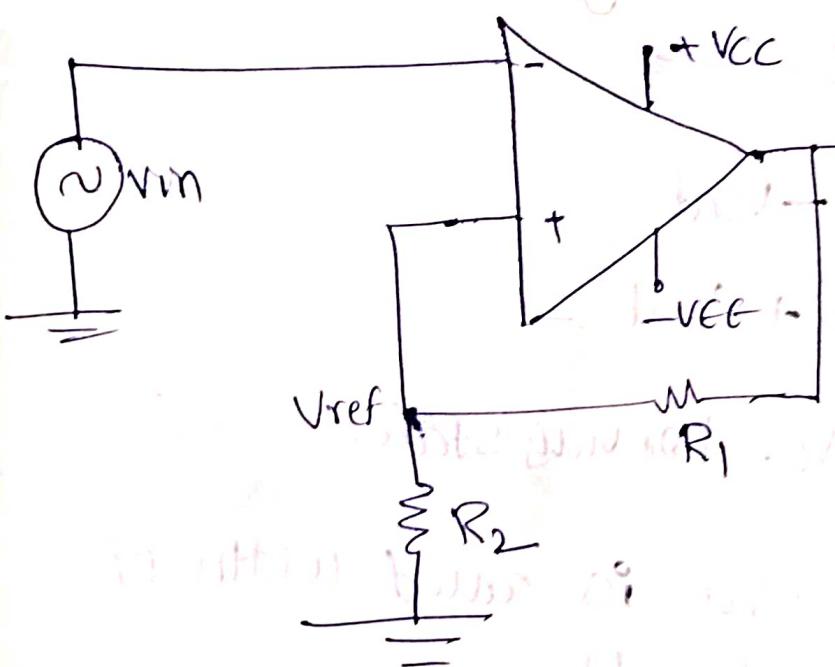⇒ The ckt diagram of Inverting schmitt trigger As shown in the fig.



Here, R_1 & R_2 forms the voltage divider which is used to generate the reference voltage.

⇒ we know that $V_{in} > V_{ref} \rightarrow V_o = -V_{sat}$

• $V_{in} < V_{ref} \rightarrow V_o = +V_{sat}$

• Ref. Voltage controlled by the R_1 & R_2 Resistors.

$$+V_{ref} = \frac{V_0}{R_1 + R_2} \cdot R_2 = \frac{+V_{sat}}{R_1 + R_2} \cdot R_2 \rightarrow \text{positive saturation}$$

$$-V_{ref} = \frac{V_0}{R_1 + R_2} \cdot R_2 = \frac{-V_{sat}}{R_1 + R_2} \cdot R_2 \rightarrow \text{negative saturation}$$

$\Rightarrow +V_{ref}$ is for positive saturation when $V_0 = +V_{sat}$ and is called upper threshold voltage (V_{UT})
[$+V_{sat}$ to $-V_{sat}$]

$\Rightarrow -V_{ref}$ is negative saturation when $V_0 = -V_{sat}$ and is called lower threshold voltage (V_{LT})
[- V_{sat} to $+V_{sat}$]
Based on these two voltages our output will be

After input & output waveform:

* $V_{in} > V_{UT} \rightarrow V_0 = -V_{sat}$

* $V_{in} < V_{LT} \rightarrow V_0 = +V_{sat}$

* $V_{LT} < V_{in} < V_{UT} \rightarrow V_0 = \text{Previous state}$

The diff b/w V_{UT} & V_{LT} is called width of hysteresis. denoted by H .

Hysteresis is also called dead band or dead zone.

$$H = \frac{2 V_{sat} R_2}{R_1 + R_2}$$

(2) $V_{id} = \underline{V_{ref}} - V_{in}$

$$\begin{aligned} V_{id} &= +V_{LT} - V_{in} \\ V_{id} &= -3 - (-u) \\ &= +ve = +V_{sat} \end{aligned}$$


* Working:-

The input and o/p wave forms of schmitt trigger As shown in fig.

* Procedure:-

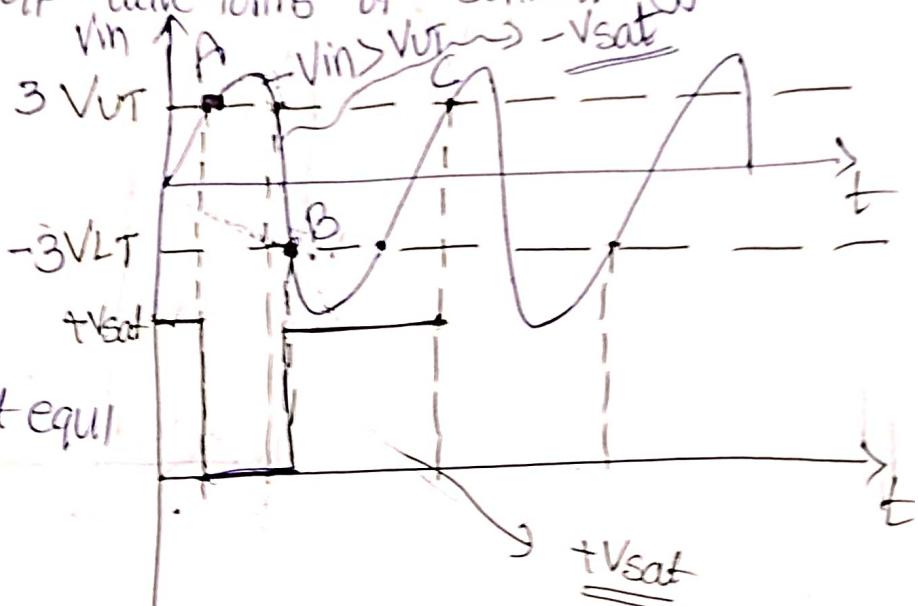1) Assume output equal to $+V_{sat}$, A

$$2) \therefore V_{UT} = \left(\frac{R_2}{R_1 + R_2} \right) + V_{sat}$$



① $V_{in} > V_{ref}$. V_{id} is $-ve$ so $V_o = -V_{sat}$


② therefore Reference voltage changes to V_{LT}

④ As long As $V_{in} > V_{ref}$ the V_o continues to be equal to $-V_{sat}$

⑤ As soon As $V_{in} < V_{ref}$ i.e V_{LT} the out o/p voltage will switch to $+V_{sat}$

* Transfer Characteristics (The graph b/w input voltage and output voltage)

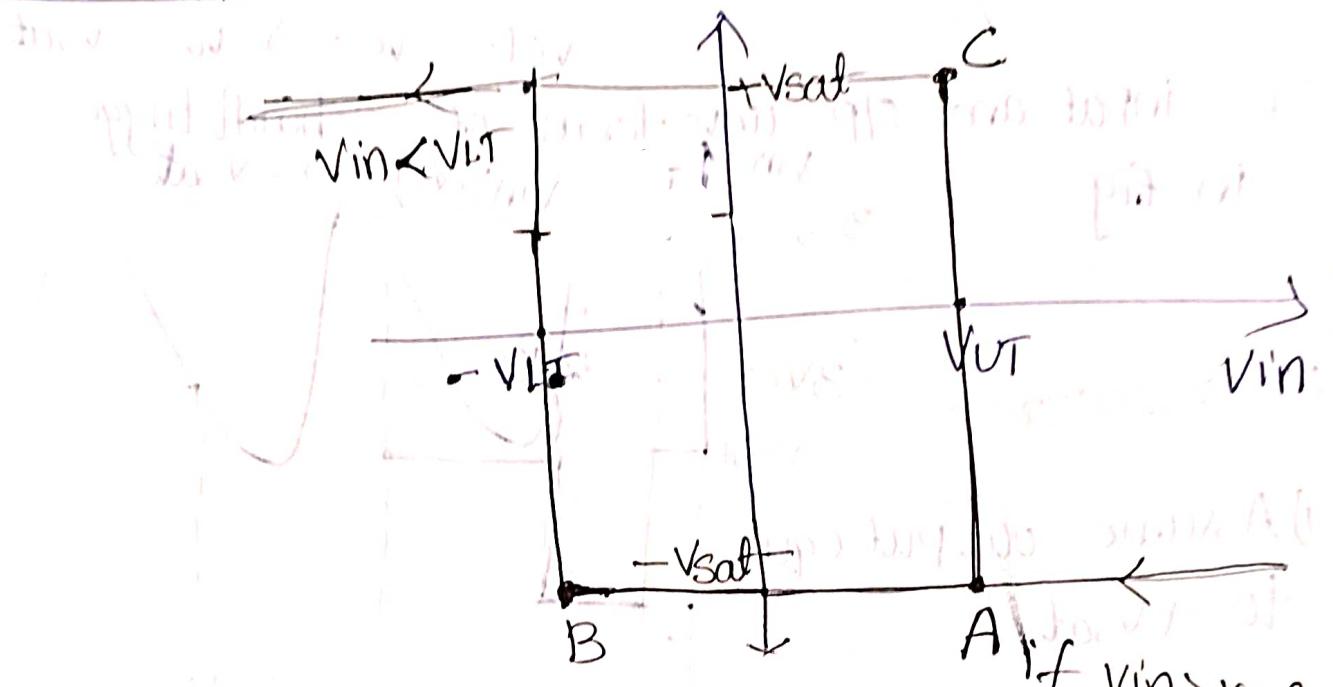* Due to feedback the comparator is said to exhibit "hysteresis"



$$V_{in} < V_{LT} \quad \text{if } V_{in} < V_{LT}$$

$$V_{in} > V_{UT} \quad \text{if } V_{in} > V_{UT}$$

⇒ The interval $V_{LT} < V_{in} < V_{UT}$ is called deadzone or dead band. This dead band condition is defined by hysteresis.

$$\therefore H = V_{UT} - V_{LT} = \frac{+V_{sat} R_2}{R_1 + R_2} - \frac{-V_{sat} R_2}{R_1 + R_2}$$

$$H = \frac{2V_{sat} R_2}{R_1 + R_2}$$