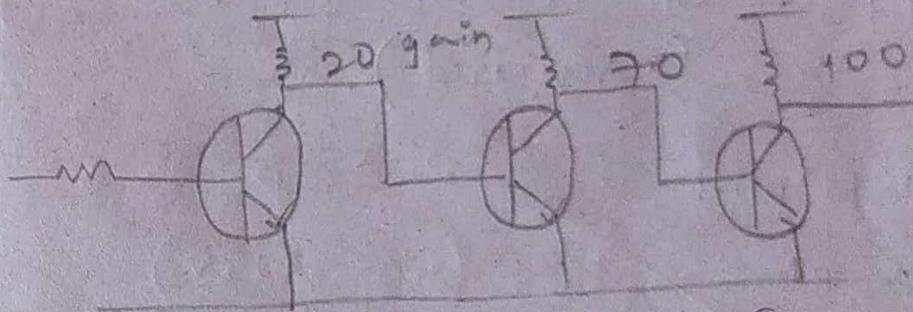


04. Operational Amplifier.

Introduction :-

- ①+ Operational Amplifier provides much more i/p impedance compared to MOSFET & BJT.
- ②+ It also provides max. gain compared to MOSFET & BJT.

Block ckt. :-



Combination of amplifiers - O.A.

- ③ Operational Amplifier eliminates noise in input signal unlike MOSFET/BJT. ; it performs mathematical operations.

Definition : Operational Amplifier is an active device which performs some mathematical operations like addition, subtraction, multiplication, integration & differentiation along with amplifying the signal.

Advantages :

- * High i/p impedance
- * High gain
- * Eliminates noise signal.

IC (Integrated circuit) : A single silicon chip on which all active & passive elements are fabricated.


* PC 741 - Operational Amplifier or Op-Amp (* required).

7 - total pins

4 - i/p pins

1 - o/p pin

* Block Diagram of OP-Amp.

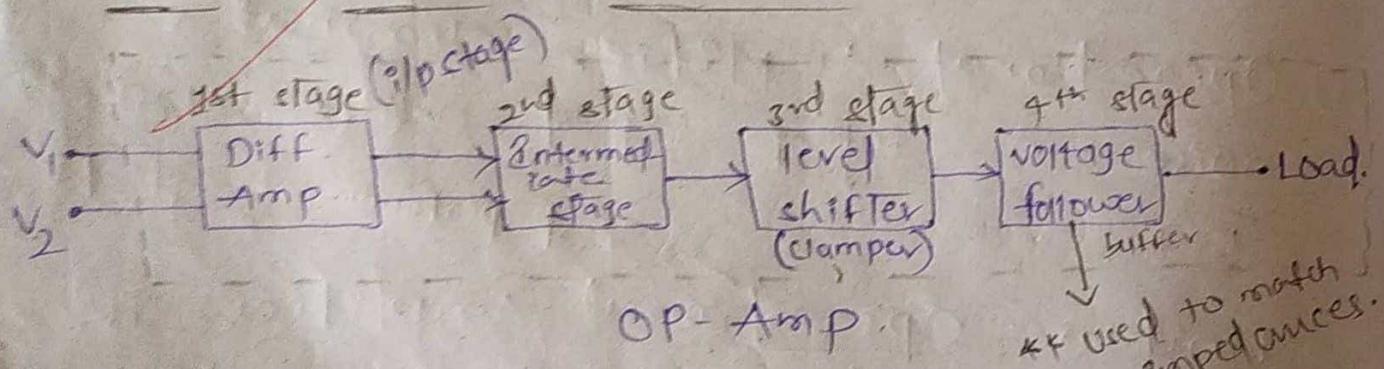


1st stage :

Differential Amp : Amplifies difference b/w two i/p signals.

ext.
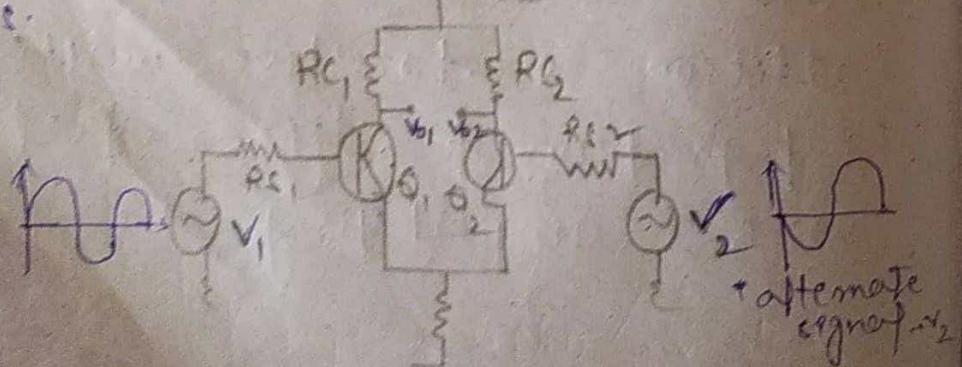
$$\begin{aligned} V_1 &= 5 \\ V_2 &= 3 \\ V_1 - V_2 &= 2 \end{aligned}$$



Diff-amp is of 4 types :-

- ① Dual i/p balanced o/p \rightarrow o/p at both capacitors
- ② Dual i/p unbalanced o/p \rightarrow o/p at any capacitor.
- ③ Single i/p balanced o/p
- ④ Single i/p unbalanced o/p.


* In this stage we use Dual i/p balanced o/p.

2nd stage :-

Intermediate stage

* In this stage we use Dual i/p unbalanced o/p.

+ output

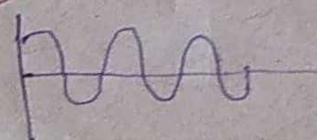

3rd stage :-

level shifter

clamper / DC restorer.

(* high impedance output
we get)


4th stage :-

voltage follower


+ Buffer ckf to transform
max power.

* allows high i/p impedance and gives
low o/p impedance signal. This
satisfies max. power transformation Theorem.

IC 741 - OP-Amp - Pin diagram:

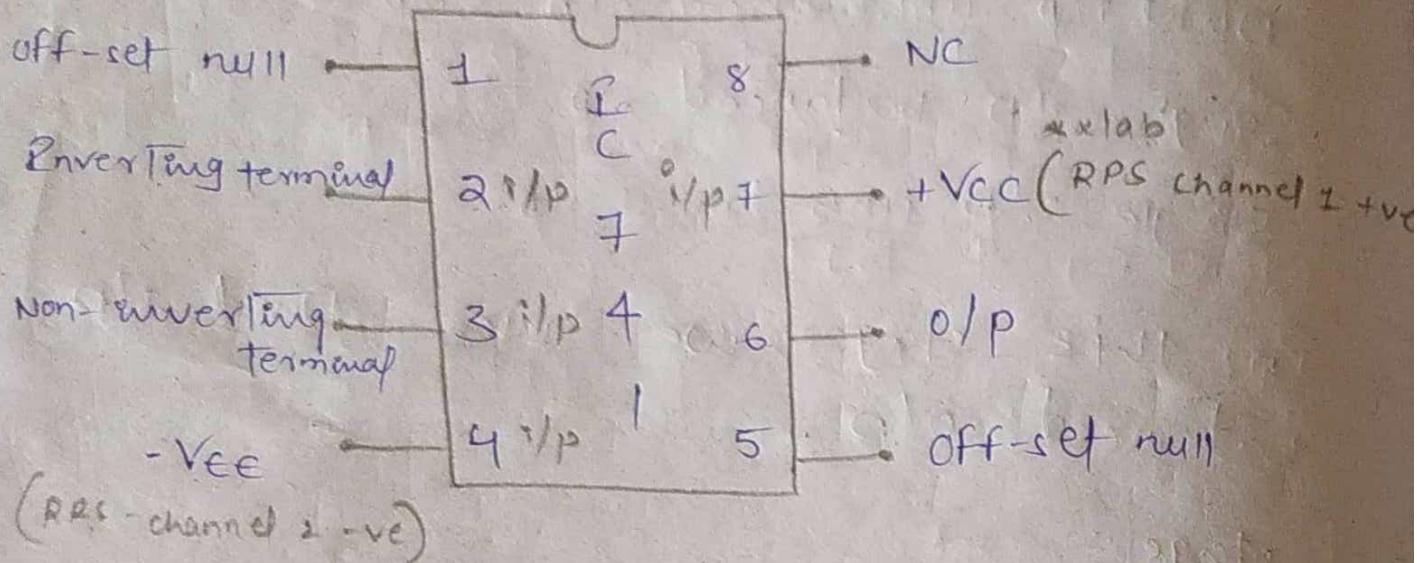

Symbol Diagram of OP-Amp:

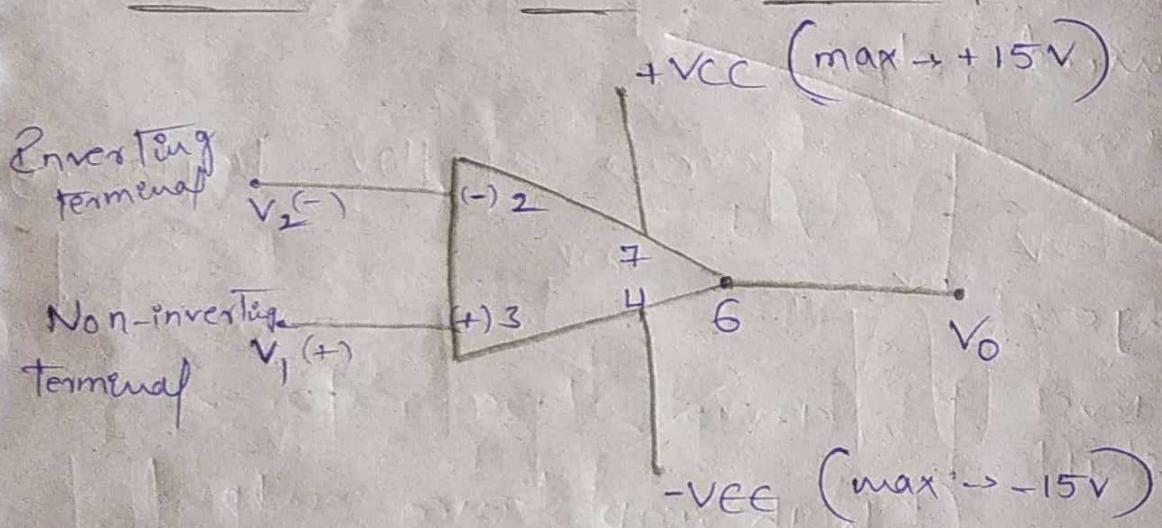

$$V_o \propto (V_1 - V_2)$$

$$V_o = A(V_1 - V_2)$$


↓
gain

case 1: $V_2 = 0$.

$$V_o = A(V_1 - 0)$$

$$= A \cdot V_1$$

$$V_o = V_1$$

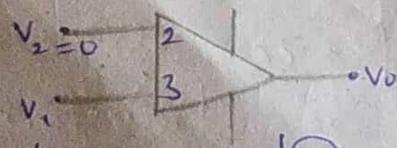

A
i/p

A
o/p



⇒ Non-inverted (pin-3)

case 2: $V_1 = 0$

$$V_o = A(0 - V_2)$$

$$V_o = -AV_2$$


$$V_o = -V_2$$

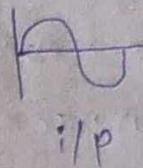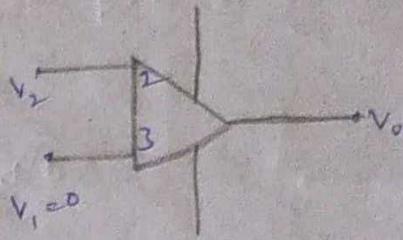

\rightarrow inverted
(Pin-2)


Characteristics of OP-Amp:

① Input-offset voltages:

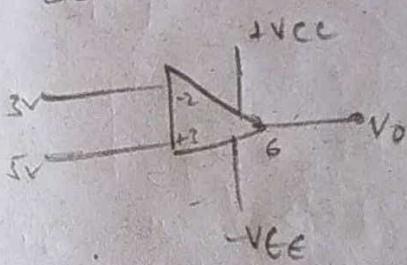

$$V_o = A(V_1 - V_2)$$

$$V_o \approx 2(5 - 3)$$

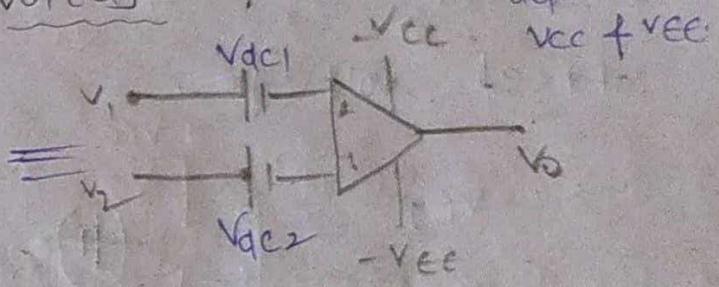

$$V_{IOE} = |V_{dc2} - V_{dc1}|$$

* To remove the unnecessary voltage we use


input-offset

voltages - $\frac{V_{dc1}}{V_{dc2}}$

not i/p voltages.


② Input-offset currents:

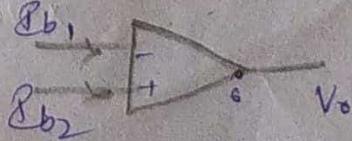* Similar to voltages to remove unnecessary current at o/p side, we use R_{b1} & R_{b2} .



$$R_{Ioc} = |R_{b1} - R_{b2}|$$

③ Input bias current :

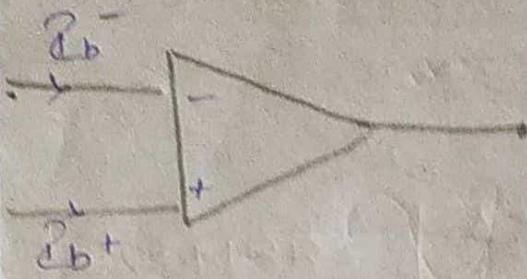


$$I_b = \frac{I_{b-} + I_{b+}}{2}$$


cancel concept for removing unnecessary current.

④ Output offset voltage :

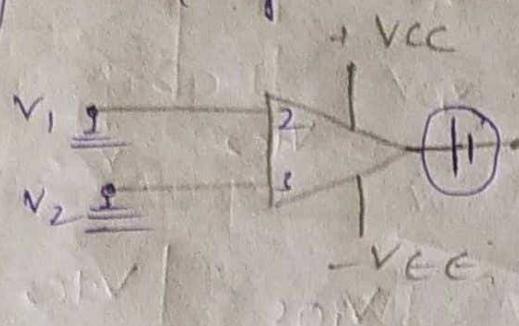Some D.C voltage is present at o/p side of OP-AMP is called output offset voltage.



⑤ Output voltage swing :

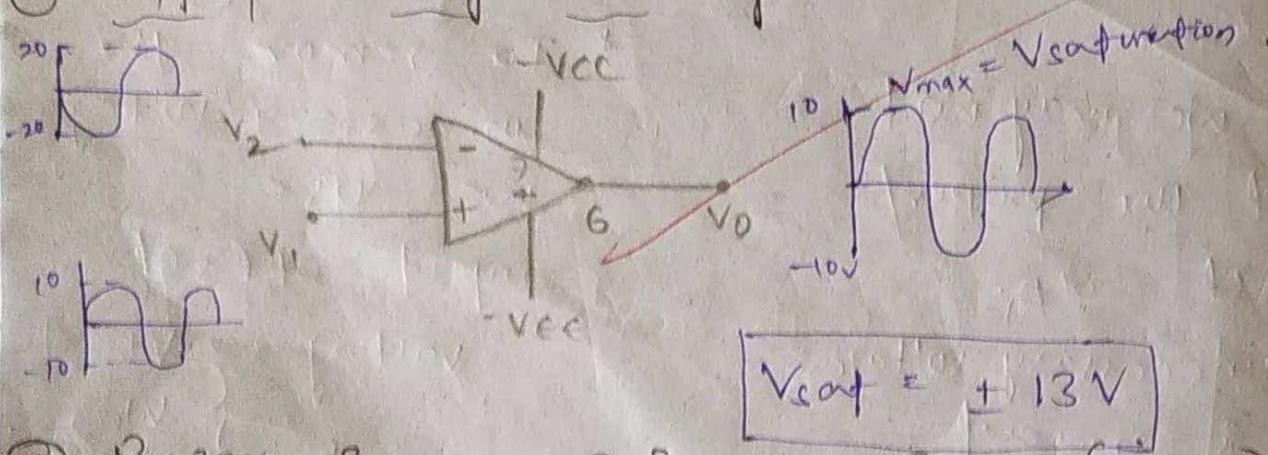

$$V_{out} = \pm 13V$$

⑥ Power Supply Rejection Ratio (PSRR) :

Ratio of input offset voltage to the change in +ve power supply.

$$PSRR = \left| \frac{\Delta V_{ios}}{\Delta V_{CC}} \right| \quad V_{CC} = \text{constant}$$

$$(or) PSRR = \left| \frac{\Delta V_{ios}}{\Delta V_{CC}} \right| \quad V_{CC} = \text{constant}$$

Ex:

$$V_{CC} = 8V \rightarrow V_{TOS} = 2mV$$

$$V_{CC} = 9V \rightarrow V_{TOS} = 2.5mV$$

$$PSRR = \frac{0.5mV}{1V} = 0.5mV$$

(7) Thermal Drift:

- ① Thermal voltage drift = The max rate of change in V_{TOS} due to change in unit temperature.


$$\frac{dV_{TOS}}{dt}$$

② Thermal drift R_{TOS} :

③ Thermal drift R_b :


If V_{VOS} , V_{TOS} , R_b are not constant. They changes due to temp.

Differential Amp:

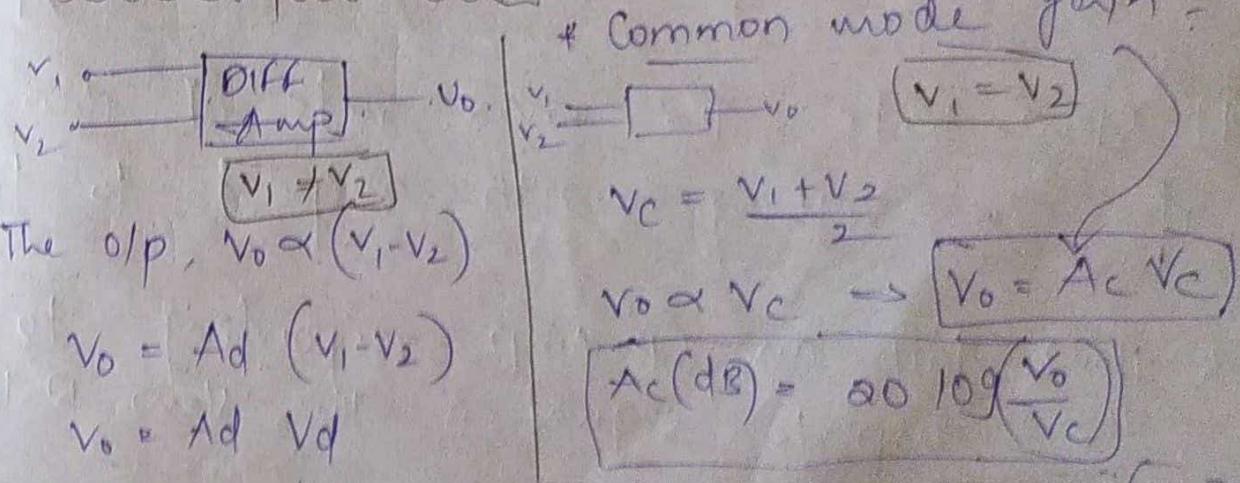

"Ad = Differential gain = $\frac{v_o}{V_d} = Ad(dB) = 20 \log \left(\frac{v_o}{V_d} \right)$
(decibels) $\rightarrow [dB]$

⑧ CMRR (Common mode Rejection Ratio).

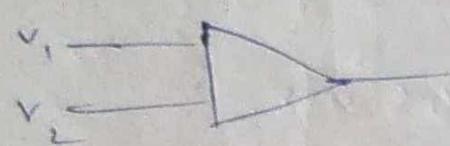

$v_o = AdVd$ (always for OP-amp)

$$CMRR = \left| \frac{Ad}{Ac} \right|.$$

* for an ideal OP-Amp, $Ac = 0$.

* For good performance of Diff. amplifier,

$$CMRR = \frac{Ad}{0} = \infty$$

* For OP-Amp, $v_o = Ad Vd$

* For Diff-Amp, $v_o = Ad Vd + Ac Vc$.

$$v_o = Ad Vd \left(1 + \frac{Ac Vc}{Ad Vd} \right)$$

$$\approx Ad Vd \left(1 + \frac{1}{\frac{Ad}{Ac}} \cdot \frac{Vc}{Vd} \right)$$


$$v_o = Ad Vd \left(1 + \frac{1}{CMRR} \cdot \frac{Vc}{Vd} \right)$$

⑨ * Slew-Rate: The max. rate of change of o/p voltage with respect to time

* How fast an OP-Amp is responding to the input signal is the Slew-Rate.

$$S = \frac{dV_{op}}{dt} \text{ volt/sec.}$$

① Ideal - OP-Amp

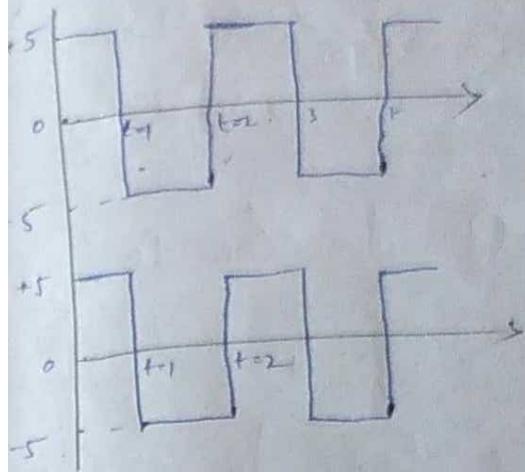


* Ideal op-Amp immediately responds to 1/p signal.

$$* \Delta t = 0.$$

$$s = \frac{dV_o}{0} = \infty \Rightarrow \text{speedy responding}$$


② practical - OP-Amp

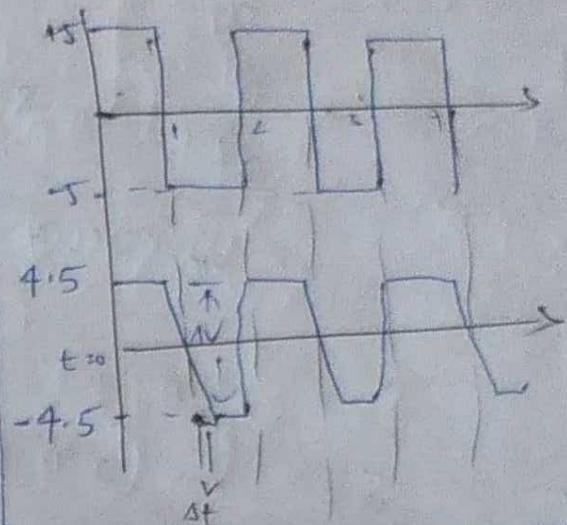

* There is some time delay Δt .

4

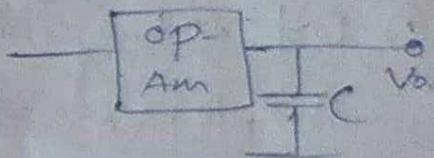
$$s = \frac{dV_o/p}{dt} = \frac{I_{C\max}}{C}$$



+ in terms of capacitance.

* Effect of slew on Sinusoidal signals.

* consider ideal Op-Amp.

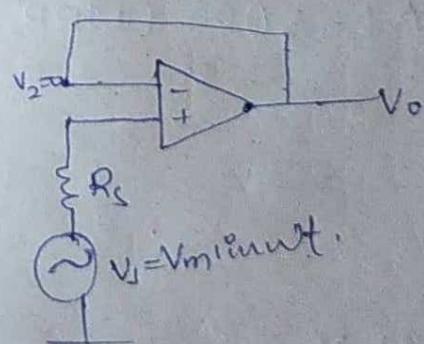

The opAmp,

$$V_o = A(V_i - V_2)$$

$$V_2 = 0, V_i = V_s, A = 1$$

$$V_o = 1(V_s)$$

$$V_o = V_s = V_m \sin(\omega t).$$

$$\text{Now, } S = \frac{dv_o}{dt} \\ = \frac{d}{dt} (V_m \sin \omega t) \\ = V_m \cos \omega t \cdot \omega$$

$$S = V_m \cdot \omega$$

$$S = V_m (2\pi f)$$

$$f_{\max} = \frac{S_{\max}}{2\pi V_m}$$

* for achieving S_{\max} , frequency should be max.

Problem :-

① Determine the o/p voltage of Differential Amplifier for i/p of 300 mV & 240 mV.

The diff. gain of the amplifier is 5000 and the value of the CMRR is 100.

Sol:- Given, for Diff. Amp,

$$v_1 = 300 \mu V, v_2 = 240 \mu V, A_d = 5000, (\text{CMRR} = 100)$$

We know that

$$\text{diff } v_o = A_d v_d + A_c v_c$$

$$v_d = v_1 - v_2 = 300 - 240 = 60 \mu V.$$

$$v_c = \frac{v_1 + v_2}{2} = \frac{300 + 240}{2} = 54^\circ = 270 \mu V.$$

We know that, $CMRR = \frac{Ad}{AC}$

$$100 = \frac{5000}{AC}$$

$$AC = \frac{5000}{100} = 50$$

$$\text{Now, } V_o = Ad V_d + Ac V_c$$

$$= (5000 \times 60 \times 10^{-6}) + (50 \times 270 \times 10^{-6})$$

$$= (300000 \times 10^{-6}) + ((27 \times 5) \times 10^2 \times 10^{-6})$$


$$= (3 \times 10^{-1}) + ((27 \times 5) \times 10^{-4})$$

$$= 0.3135 \text{ V}$$

$$V_o = 313.5 \text{ mV}$$

② If the base currents for Emitter coupled transistor of a Diff. Amp is 18.4 A & 22.4 A. Determine

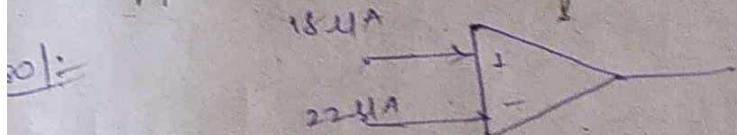① i/p bias current & i/p off-set current.



$$I_{b1} = 18.4 \text{ A}, I_{b2} = 22.4 \text{ A}$$

$$\text{② I/p bias current } (I_b) = \frac{I_{b1} + I_{b2}}{2}$$

$$= \frac{22.4 + 18.4}{2} = 20.4 \text{ A}$$

$$\text{③ I/p off-set current } (I_{bo}) = |I_{b1} - I_{b2}|$$

$$= |18.4 - 22.4|$$

$$= 4 \text{ A}_q$$

③ An Op-Amp operates as unity gain buffer with 3V(p-p) square wave i/p. If Op-Amp is ideal with slew rate $0.5 \text{ V}/\mu\text{sec}$ find the max. frequency of operation.

$$\text{Sol: } V(\text{p-p}) = 2V_m \\ V_m = \frac{V(\text{p-p})}{2} \\ \approx \frac{3}{2} = 1.5 \text{ V.}$$

$$f_m = \frac{S}{2\pi V_m} \\ = \frac{0.5}{2\pi \times 15 \times 10^{-6}} \\ \approx 53 \text{ kHz}$$


We know, $f_{\max} = \frac{S_{\max}}{2\pi \times V_m}$

$$= \frac{0.5 \text{ V}/10^{-6} \text{ s}}{2\pi \times 1.5} \\ \approx \frac{0.5}{2\pi \times 1.5 \times 10^{-6}}$$


$$f_{\max} \approx 53.07 \text{ kHz.}$$

05. Applications of OP-Amp.

Open loop OP-Amp

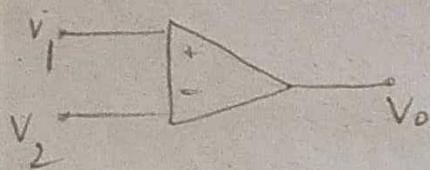


Closed OP-Amp

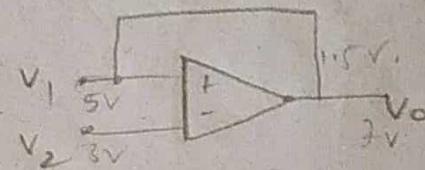

Ex:- Comparator
ckt


-ve feedback

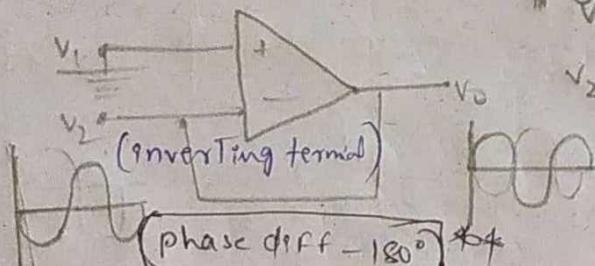

Ex:- Used in out-off phase

Amplifiers,
filters.

+ve feedback

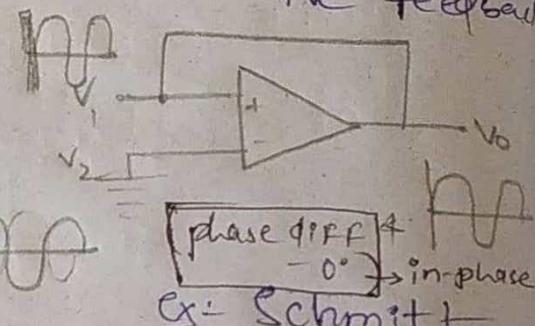

Ex:- Schmitt
trigger.

* Compared to closed OP-Amp, Open loop OP-Amp gives high gain.


Open loop OP-Amp :-

① Inverting OP-Amp

$V_1 = 0, V_2 = V_{in}$ (considering resistances very small)
We know that,


$$V_o = Ad V_d \\ = Ad (V_1 - V_2)$$

$V_o = -Ad V_{in}$

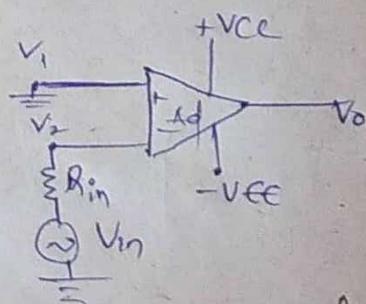

(source connected -ve
(inverting terminal))

wave forms: ($A_d = 1$).

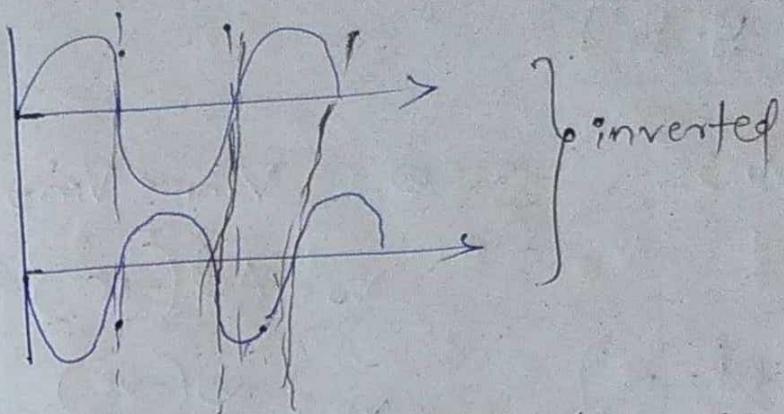



② Non Inverting OP-Amp :

$$v_1 = V_{in}, v_2 \approx 0.$$


$$V_o = A_d (V_{in} - 0)$$

$$\boxed{V_o = A_d V_{in}}$$

o/p waveforms :

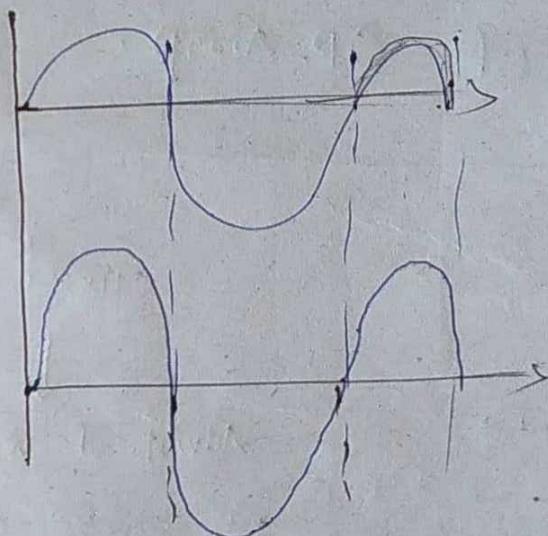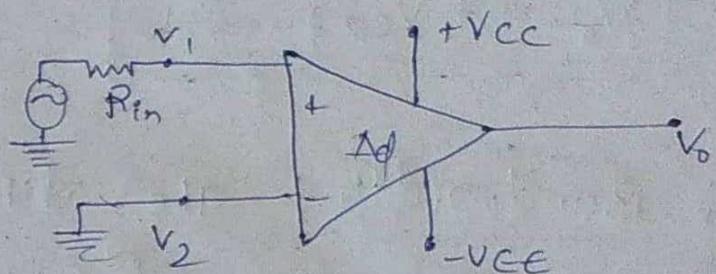

③ Differential OP-Amp :

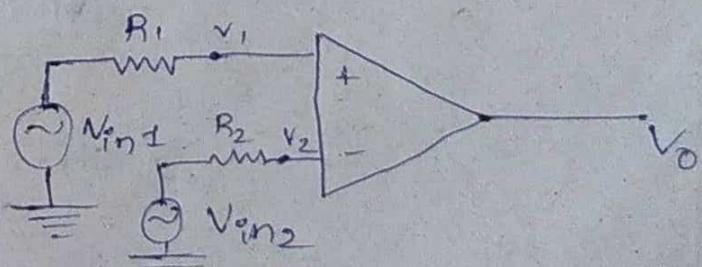

considering R ideal ($A_d = \infty$).

$$V_1 = V_{in1}, \quad V_2 = V_{in2}$$

$$V_o = Ad \cdot V_d = Ad(V_{in1} - V_{in2})$$

case ① : $V_{in1} > V_{in2}$

$$V_o = Ad(+ve)$$

$$V_o = \infty(+ve) (\because Ad = \infty) \\ (\text{ideal})$$

$$V_o \approx +V_{saturation}$$

case ② : $V_{in1} < V_{in2}$

$$V_o = Ad(-ve)$$

$$V_o = \infty(-ve)$$

$$\boxed{V_o = -V_{sat}}$$

* Bandwidth: The difference b/w higher cutoff freq & lower cutoff freq.

* Without bandwidth, signal can't be transmitted.

Applications of OP-Amp

Open loop

+ Limitations:

1. Offers max. gain but can't be controlled.
2. Gain is temp dependent
3. Offers small bandwidth


Closed loop

Advantage of -ve feedback

1. can be controlled
2. Increases bandwidth
3. Offers high i/p impedance
4. Offers low o/p admittance
5. Temp independent

* Virtual Ground Concept:

** only valid for ideal OP-Amp

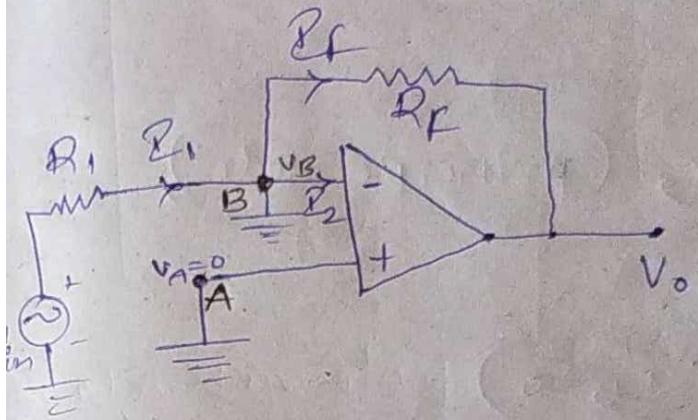

* for ideal OP-Amp:
(non-unity)
Gain $A_d = \infty$
 $R_i = \infty$
 $CMRR = \infty$
 $R_o = 0$

$$v_o = A_d v_{in}$$


$$= A_d (v_B - v_A)$$

$$v_A =$$

* Closed Loop OP-Amp Configurations:

① Inverting closed loop OP-Amp:

ckt diagram:

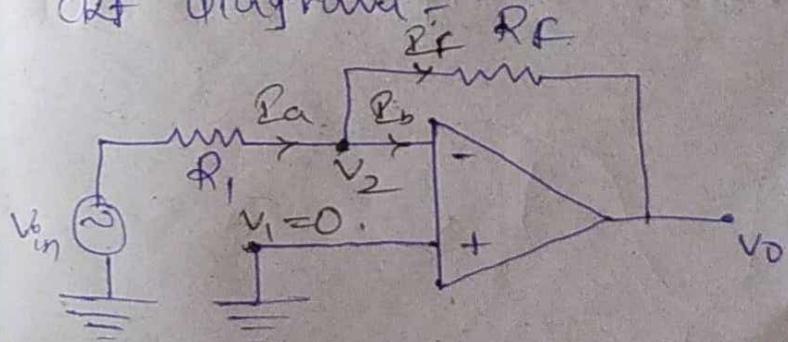

Calculation of o/p voltage expr:

Acc to virtual ground concept,

$$V_1 = V_2 = 0.$$

Apply KCL at V_2 (principle node),

$$R_a - R_b - R_f = 0$$

$$R_a - R_f = 0 \quad (\because R_b \approx 0)$$

$$R_a = R_f$$

$$\frac{V_{in} - V_2^o}{R_i} = \frac{V_2 - V_o}{R_f} \quad (\therefore \text{By Ohm's law}).$$


$$\frac{V_{in} - 0}{R_i} = \frac{0 - V_o}{R_f}$$

$$\frac{V_{in}}{R_i} = -\frac{V_o}{R_f}$$

$$V_o = -\frac{R_f}{R_i} V_{in}$$


$$\boxed{\text{Gain} = \frac{V_o}{V_{in}} = -\frac{R_f}{R_i}}$$

waveforms:

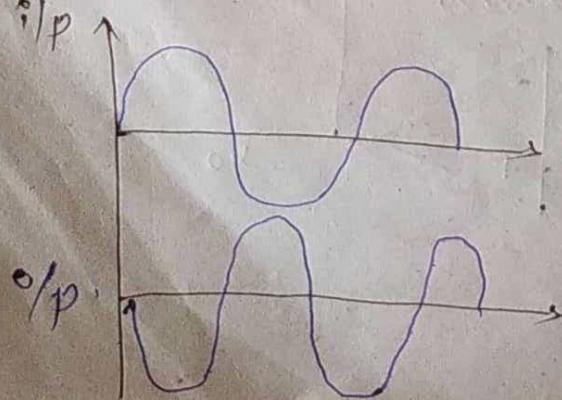

* Non-Inverting Amplifier:

The CKT diagram of non-inverting amp

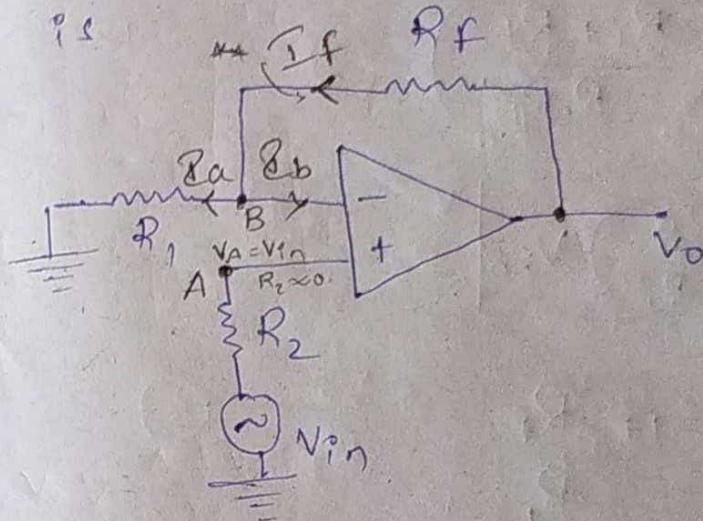

Calculation of o/p voltage:

→ Acc. to virtual Ground concept,

$$V_A = V_B = V_{in}$$

→ Applying KCL at principle (B) node,

$$R_f - R_a - R_b = 0 \quad (\because R_b = 0).$$

$$R_f - R_a = 0$$

$$R_f = R_a \quad \text{--- (1)}$$

→ Acc. to Ohm's law,

$$I_a = \frac{V_B - 0}{R_1} = \frac{V_{in}}{R_1} \quad \text{--- (2)}$$

$$I_f = \frac{V_o - V_B}{R_f} = \frac{V_o - V_{in}}{R_f} \quad \text{--- (3)}$$

Sub. eq (2) + (3) in (1).

$$\frac{V_o - V_{in}}{R_f} = \frac{V_{in}}{R_1}$$


$$\frac{V_o}{R_f} = \frac{V_{in}}{R_i} + \frac{V_{in}}{R_f}$$

$$\frac{V_o}{R_f} = V_{in} \left(\frac{R_i + R_f}{R_i R_f} \right)$$

$$\therefore V_o = \left(1 + \frac{R_f}{R_i} \right) V_{in}$$

$$\frac{V_o}{V_{in}} = A_d = 1 + \frac{R_f}{R_i}$$

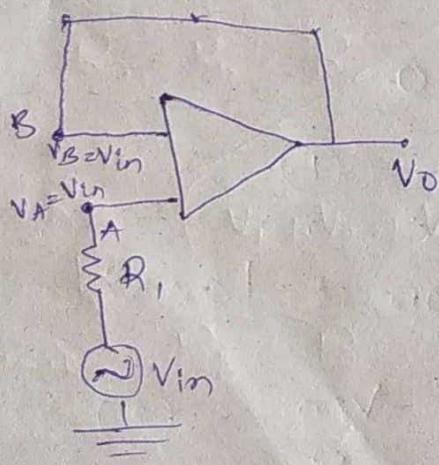* Voltage Follower : (Buffer - doesn't amplify signal).
 The ckt in which o/p follows the i/p signal is called 'voltage follower ckt'.



\Rightarrow Acc. to virtual Ground

$$V_A = V_B = V_{in}$$


$$\therefore V_o = V_{in}$$

* Basic Operations of OP-Amp :

- * Basically OP-Amp is designed for obtaining max. gain.
- * But it also used to perform some operations like -
 - Addition @ summation - Inverting Adder
 - Subtraction @ Difference Non-Inverting Adder.
 - Multiplication
 - Integration, Differentiating
 - Comparator.

* Inverting Adder:

- The circuit diagram is

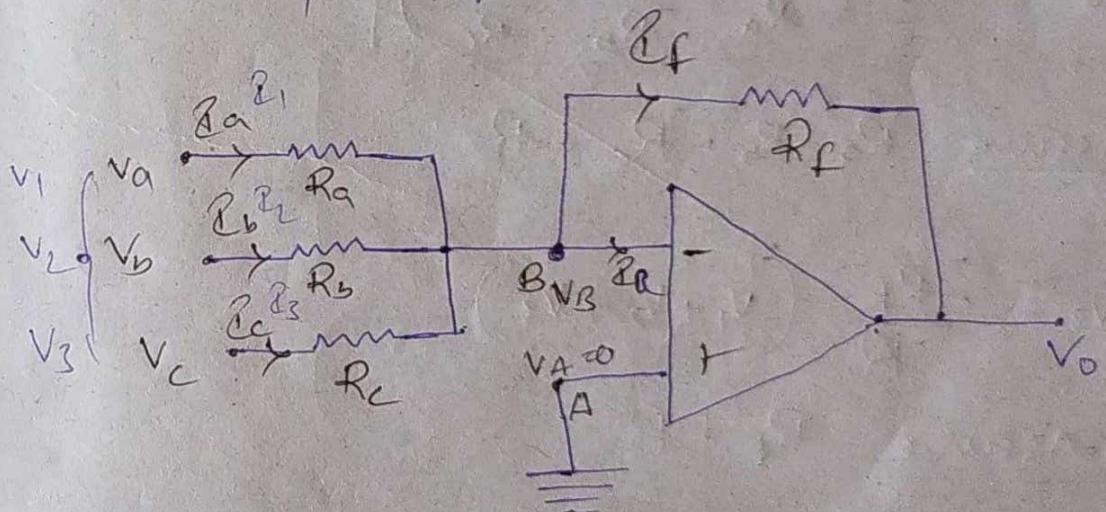

⇒ Acc. to Virtual Ground,

$$V_A = V_B = 0$$

→ Applying KCL at principle node,

$$I_{O1} + I_{R2} + I_{R3} - I_f - I_a = 0$$

$$R_1 + R_2 + R_3 = R_f - \textcircled{1}$$

\Rightarrow Acc. to Ohm's law,

$$I_1 = \frac{V_1 - V_B}{R_a} = \frac{V_1 - 0}{R_a} = \frac{V_1}{R_a} \quad \textcircled{2}$$

$$I_2 = \frac{V_2 - V_B}{R_b} = \frac{V_2 - 0}{R_b} = \frac{V_2}{R_b} \quad \textcircled{3}$$

$$I_3 = \frac{V_3 - V_B}{R_c} = \frac{V_3 - 0}{R_c} = \frac{V_3}{R_c} \quad \textcircled{4}$$

$$I_f = \frac{V_B - V_o}{R_f} = \frac{0 - V_o}{R_f} = -\frac{V_o}{R_f} \quad \textcircled{5}$$

Sub. $\textcircled{2} \textcircled{3} \textcircled{4} \textcircled{5}$ in $\textcircled{1}$,

$$\frac{V_1}{R_a} + \frac{V_2}{R_b} + \frac{V_3}{R_c} = -\frac{V_o}{R_f}$$

$$\boxed{V_o = -R_f \left(\frac{V_1}{R_a} + \frac{V_2}{R_b} + \frac{V_3}{R_c} \right)}$$


\hookrightarrow Assume $R_a = R_b = R_c = R$

$$V_o = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

\Rightarrow Assume $R_f = R$.

$$\boxed{V_o = -(V_1 + V_2 + V_3)}$$

* Non-inverting Adder:

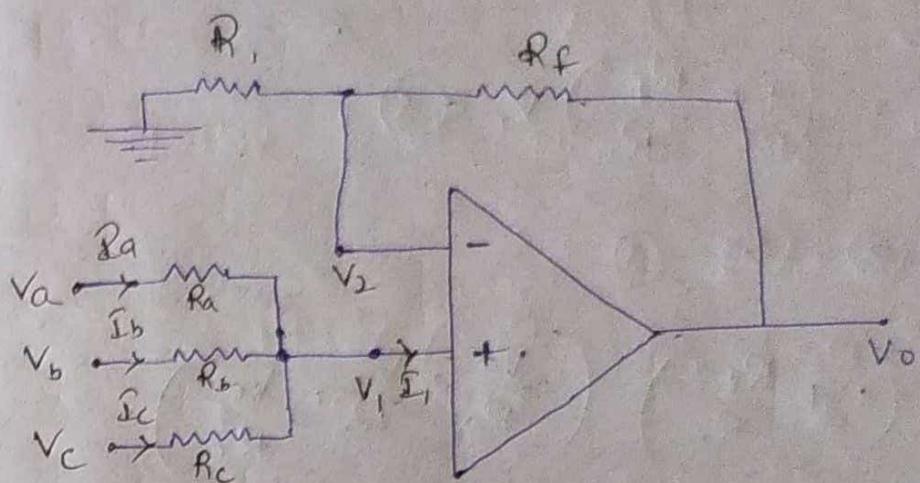

* The o/p voltage V_o :-

Apply KCL at Node

$$R_a + R_b + R_c - R_i = 0$$

$$R_a + R_b + R_c = 0 \quad (\because R_i \approx \infty)$$

→ Acc. to Ohm's law,

$$R_a = \frac{V_a - V_1}{I_a}, \quad R_b = \frac{V_o - V_1}{I_b}, \quad R_c = \frac{V_c - V_1}{I_c}$$

R_a, R_b, R_c sub eq. ①

$$\frac{V_a - V_1}{R_a} + \frac{V_b - V_1}{R_b} + \frac{V_c - V_1}{R_c} = 0$$

$$\begin{aligned} \frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} &= \frac{V_1}{R_a} + \frac{V_1}{R_b} + \frac{V_1}{R_c} \\ &= V_1 \left(\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c} \right) \end{aligned}$$

$$\therefore V_1 = \frac{\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c}}{\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c}}$$

→ We know, V_o of non-inverting OP-Amp

ii

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i - \textcircled{3}$$

Sub in $\textcircled{2}$ in $\textcircled{3}$.

$$\therefore V_o = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{V_a + V_b + V_c}{\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c}} \right)$$

Assume $R_a = R_b = R_c = R_i = R$.

$$\therefore V_o = \left(1 + \frac{R_f}{R}\right) \left[\frac{\frac{V_a + V_b + V_c}{R}}{\frac{1}{R} + \frac{1}{R} + \frac{1}{R}} \right]$$

$$= \left(1 + \frac{R_f}{R}\right) \left[\frac{V_a + V_b + V_c}{3} \right]$$


$$V_o = \left(1 + \frac{R_f}{R}\right) \left(\frac{V_a + V_b + V_c}{3} \right)$$

Assume $R = \frac{R_f}{2}$

$$V_o = \left(1 + \frac{R_f}{R_f/2}\right) \left(\frac{V_a + V_b + V_c}{3} \right)$$
$$= (1+2) \left(\frac{V_a + V_b + V_c}{3} \right)$$


$$\therefore V_o = V_a + V_b + V_c$$

Subtractor:

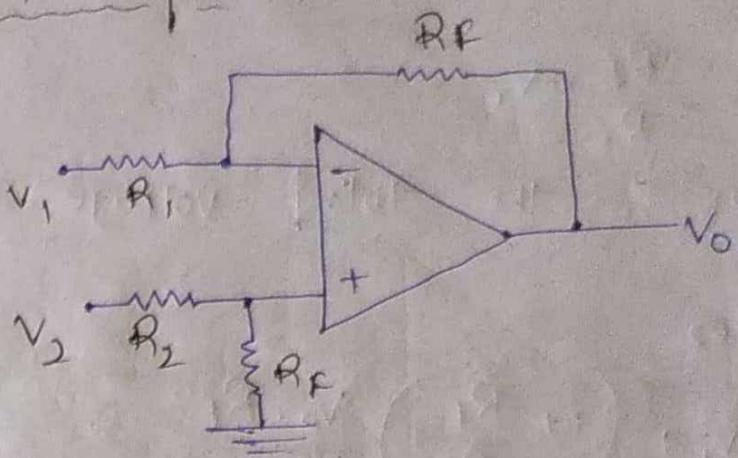

Apply Superposition theorem.

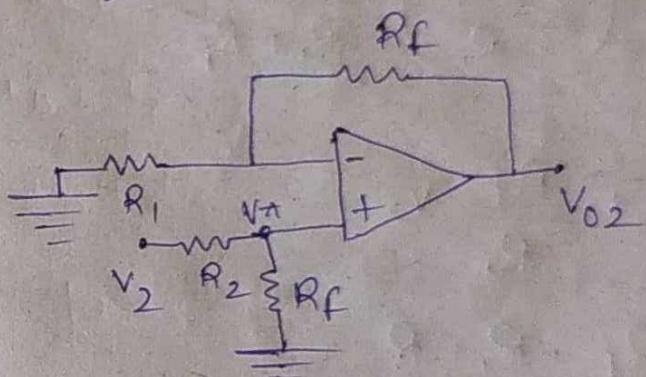Step ① : V_2 source acting alone, V_1 - short ckted.



Apply Voltage Division Rule at V_A .


$$V_A = V_2 \cdot \frac{R_f}{R_2 + R_f}$$

The non-inv op-Amp o/p volt is

$$V_{02} = \left(1 + \frac{R_f}{R_1}\right) \cdot V_A$$

$$V_{02} = \left(1 + \frac{R_f}{R_1}\right) \cdot V_2 \cdot \frac{R_f}{R_2 + R_f} \quad - \textcircled{A}$$

Step ② : V_1 acting alone, V_2 - s.c.

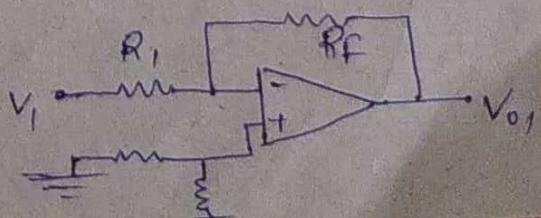

We know , inv- OPAMP o/p v_o is

$$v_{o2} = -\frac{R_f}{R_1} \cdot v_1$$

Acc. to SPT . the total voltage

$$v_o = v_{o1} + v_{o2}$$

$$= -\frac{R_f}{R_1} v_1 + \left(1 + \frac{R_f}{R_1}\right) \frac{v_2 \cdot R_f}{R_2 + R_f}$$

Assume $R_1 = R_2$

$$v_o = -\frac{R_f}{R_1} v_1 + \left(\frac{R_1 + R_f}{R_1}\right) \cdot \frac{v_2 \cdot R_f}{R_1 + R_f}$$


$$v_o = -\frac{R_f}{R_1} v_1 + \frac{R_f}{R_1} v_2$$

Assume $R_f = R_1 = R$

$$v_o = -(v_1 + v_2)$$

$$\boxed{v_o = v_2 - v_1}$$

* Logarithmic Amplifier.

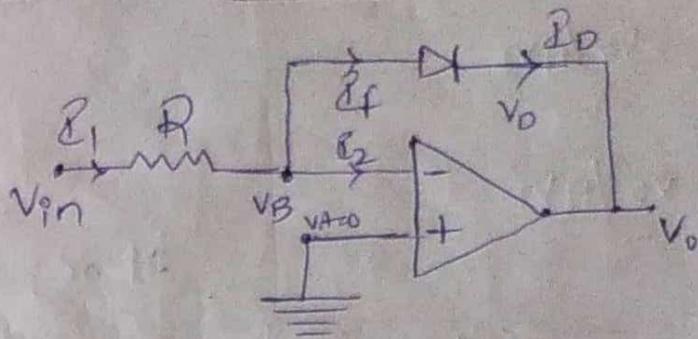

calculation of o/p voltage :-

→ Acc. to virtual GND,

$$V_A = V_B = 0$$

→ Apply KCL at principle Node

$$R_1 - R_2 - R_f = 0$$

$$R_1 - R_f = 0 \quad (\because R_2 = 0)$$

$$\boxed{R_1 = R_f} \quad \text{--- (1)}$$

→ Acc. to ohm's law,

$$R_1 = \frac{V_{in} - V_B}{R} = \frac{V_{in}}{R} \quad \text{--- (1)}$$


We know the diode current eqn. is

$$I_f = I_0 \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$I_f = I_0 e^{\frac{V_D}{nV_T}} - I_0$$

Assume $I_0 e^{\frac{V_D}{nV_T}} \gg I_0$
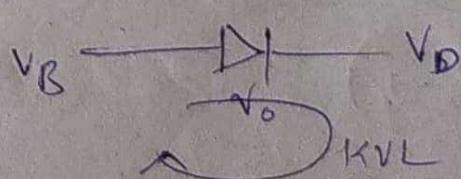
$$I_f = I_0 e^{\frac{V_D}{nV_T}} \quad \text{--- (A)}$$



$$-V_B + V_o + V_D = 0$$

$$V_D = -V_o \quad (\because V_B = 0)$$

(Sub. in (A))

$$\Rightarrow I_f = I_0 e^{-\frac{V_o}{nV_T}} \quad \text{--- (B)}$$

sub. or ③ ⑧ in ①

$$\frac{V_{in}}{R} = R_0 e^{-V_o/nVT}$$


$$\frac{V_{in}}{R_0 R} = e^{-V_o/nVT}$$

$$-V_o = n VT \ln \left(\frac{V_{in}}{R_0 R} \right)$$

Here,

$$V_o \propto \ln V_{in}$$

* Anti logarithmic Amplifiers.

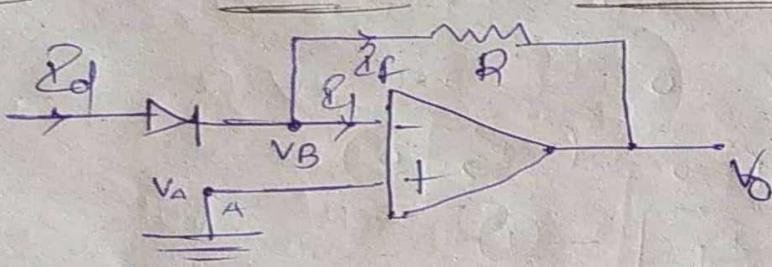

Acc. to virtual Ground concept

$$V_A \approx V_B = 0$$

Apply KCL at principle node

$$R_d - R_i - R_f = 0$$

$$R_d = R_f \quad \text{--- ①}$$

($\because R_i \approx \infty$)

Acc. to ohms law,

$$R_f = \frac{V_B - V_o}{R} = \frac{-V_o}{R} \quad \text{--- ②}$$


we know that the Diode current eqn.

$$I_d = I_0 (e^{\frac{V_d}{nVT}} - 1)$$

$$= I_0 e^{\frac{V_d}{nVT}} - I_0$$

Assume $R_o e^{\frac{V_o}{nV_T}} \gg R_o$
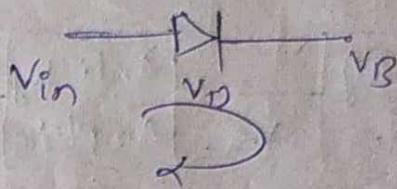
$$R_d = R_o e^{\frac{V_o}{nV_T}} - \textcircled{A}$$



Applying KVL in loop

$$-V_{in} + V_o + V_B = 0$$

$$V_o = V_{in} \quad (\because V_B = 0)$$

— sub. in \textcircled{A}

$$R_d = R_o e^{\frac{V_{in}}{nV_T}} - \textcircled{B}$$


ev \textcircled{A} \textcircled{B} sub in $\textcircled{1}$

$$R_o e^{\frac{V_{in}}{nV_T}} = -\frac{V_o}{R}$$


$$-V_o = R_o R e^{\frac{V_{in}}{nV_T}}$$

$$\boxed{V_o = -R_o R e^{\frac{V_{in}}{nV_T}}}$$

* Multiplexer

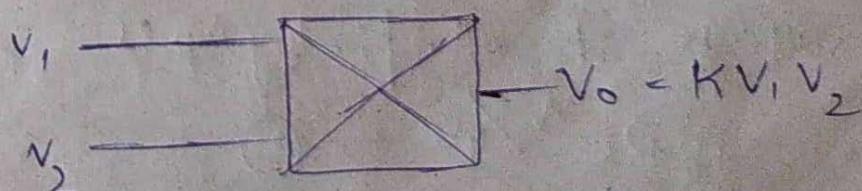

The Block Diagram of multiplier is

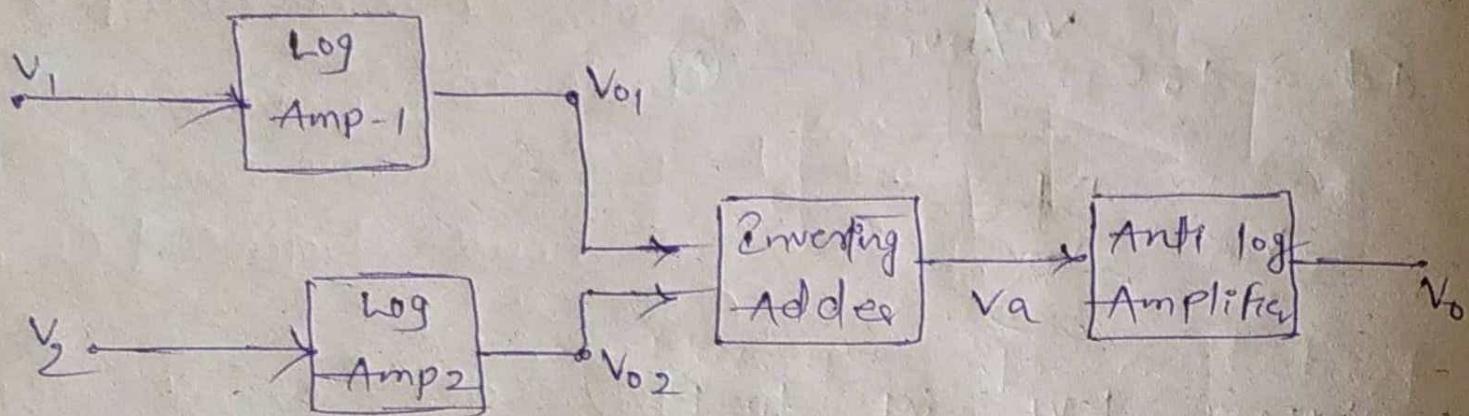

Consider log Amp - ①.

The o/p expression of voltage is

$$V_{01} = -nV_T \ln\left(\frac{V_1}{R_o R}\right)$$

consider log Amp - ②, the o/p voltage is

$$V_{02} = -nV_T \ln\left(\frac{V_2}{R_o R}\right)$$

The o/p voltage of inv. adder is

$$V_a = -(V_{01} + V_{02})$$

$$V_a = -\left[-nV_T \ln\left(\frac{V_1}{R_o R}\right) - nV_T \ln\left(\frac{V_2}{R_o R}\right)\right]$$

$$V_a = -nV_T \left(\ln\left(\frac{V_1 V_2}{R_o^2 R^2}\right) \right) \quad \textcircled{1}$$

The o/p voltage of Anti-log Amp is

$$V_0 = -R_o R e^{\frac{V_a}{nV_T}} \quad \textcircled{2}$$

sub. ex ① in ②

$$V_0 = -R_o R e^{nV_T \ln\left(\frac{V_1 V_2}{R_o^2 R^2}\right)}$$

$$V_o = -\frac{R_f}{R_i} \cdot \frac{V_1 V_2}{R_o + R_f}$$


$$V_o = -\frac{V_1 V_2}{R_o + R_f}$$

$$\boxed{V_o = K V_1 V_2}$$

(\because By considering $\frac{1}{R_o + R_f}$ as constant)

Problems:

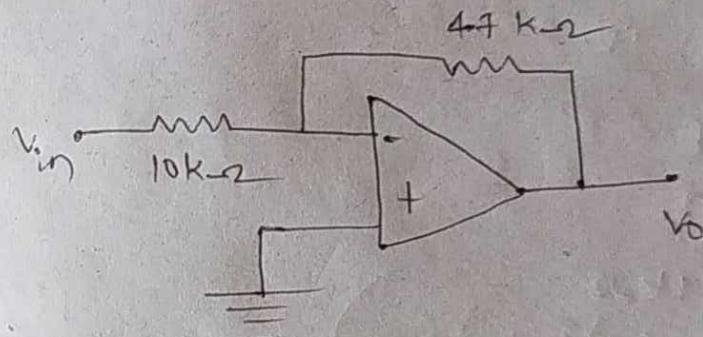- 1) Determine the voltage gain of the following OP-Amp :-



Sol:- The given OP-Amp is an Env. OP-Amp.

Given, $R_i = 10\text{k}\Omega$, $R_f = 47\text{k}\Omega$

We know that, The O/p volt of Env. OP-Amp is

$$V_o = -\frac{R_f}{R_i} \cdot V_{in}$$


$$\frac{V_o}{V_{in}} = -\frac{47 \times 10^3}{10 \times 10^3} \quad \textcircled{1}$$

$$\boxed{\frac{V_o}{V_{in}} = -4.7}$$

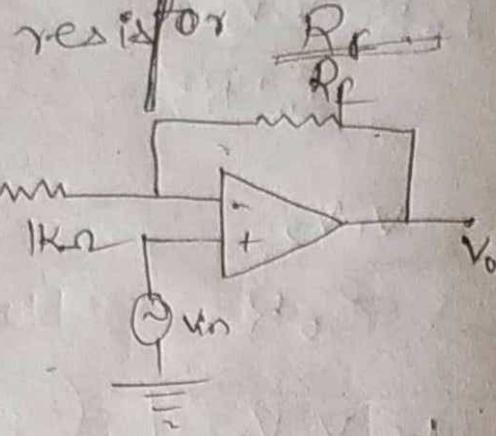2) The Gain offered by the Op-Amp is
Determine feedback resistor R_f

sol: The Given OP-Amp

is an non-inverting OP-Amp (\because Source connected to in)



We know, o/p volt is

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$

$$\frac{V_o}{V_{in}} = \left(1 + \frac{R_f}{R_i}\right)$$

$$A_d = 1 + \frac{R_f}{1 \cdot 10^3}$$


$$61 = \frac{1k\Omega + R_f}{1k\Omega}$$

$$R_f = 61k\Omega - 1k\Omega$$

$$R_f = 60k\Omega$$

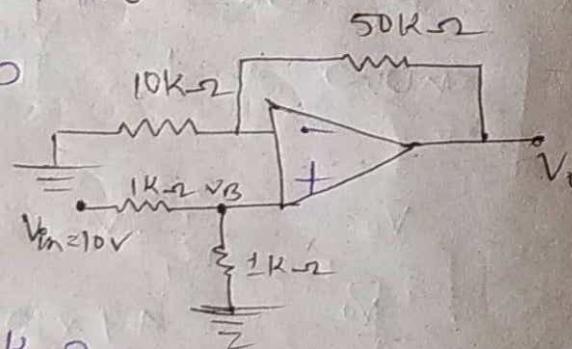3) Find the o/p voltage V_o of the following OP-A

sol: The Given OP-Amp
is an non-inverting
with i/p volt - V_B .



Given, $R_i = 10k\Omega$, $R_f = 50k\Omega$

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_B$$

$$= \left(1 + \frac{50}{10}\right) \cdot 5$$

$$= (1+5) \cdot 5$$

$$V_o = 30V$$

calc. of V_B :


apply volt. div rule

$$V_B = 10 \cdot \frac{1}{1+1} = \frac{10}{2}$$

$$= 5V$$

4) The non-inverting OP-Amp as shown in figure
Determine

- ① A_d
- ④ I_o
- ② V_o
- ③ I_L

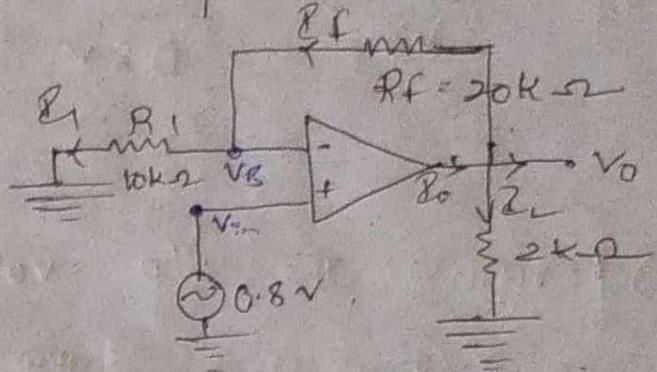

Sol: Given, $R_f = 20k\Omega$, $R_2 = 10k\Omega$, $V_{in} = 0.8V$

Acc. to virtual ground concept,

$$V_A = V_B = 0.8V$$

⑤ I_L

$$I_L = \frac{V_B - 0}{R_L} = \frac{0.8}{10 \cdot 10^3} = \frac{0.8}{10^5} = \frac{80}{10^6} = 80 \mu A$$

⑥ we know op volt. of non-inverting OP-Amp

$$\begin{aligned} V_o &= \left(1 + \frac{R_f}{R_1}\right) V_{in} \\ &= \left(1 + \frac{20}{10}\right) 0.8 = (1+2) 0.8 = (3 \times 0.8) \end{aligned}$$

$$V_o = 2.4V$$

$$+ I_f = \frac{V_o - V_B}{R_f} = \frac{2.4 - 0.8}{20 \cdot 10^3} = \frac{1.6}{20 \cdot 10^4} = \frac{8}{10^5} = 80 \mu A$$

$$⑦ I_L = \frac{V_o}{R_L} = \frac{2.4}{2 \cdot 10^3} = \frac{1.2}{10^3} = \frac{12}{10^4} = 1.2mA$$

⑧ Applying KCL at op side

$$R_o - R_f - R_L = 0$$


$$R_o = R_f + R_L = 80 \times 10^6 + 1.2 \times 10^{-3}$$

$$R_o = 1.28mA$$

$$\textcircled{1} \quad A_d = \frac{V_o}{V_{in}} = \frac{2.4V}{0.8V} = 3$$

⑤ Determine the o/p voltage for the following

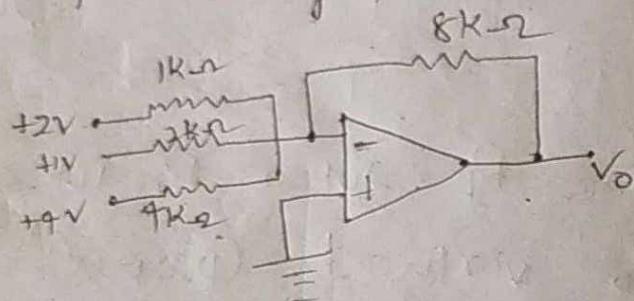Sol: The given OP-Amp is an inverting adder.



$$\text{Given, } R_1 = 1k\Omega, V_1 = 2V$$

$$R_2 = 2k\Omega, V_2 = 1V$$

$$R_3 = 4k\Omega, V_3 = 4V$$

$$R_F = 8k\Omega$$

$$\therefore V_o = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$= -8k\Omega \left(\frac{2}{1} + \frac{1}{2} + \frac{4}{4} \right)$$

$$= -8k\Omega (2 + 0.5 + 1)$$

$$= -8 (3.5)$$

$$V_o = -28V$$


⑥ Determine o/p voltage V_o for the following

Ckt:

Sol: Given, $R_F = 5k\Omega, R_1 = 1k\Omega$
we want V_A :

Apply KCL at Node V_A
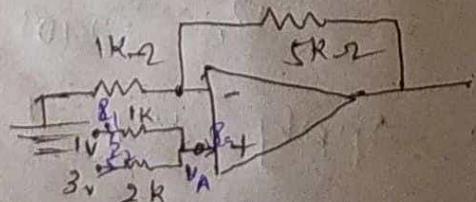
$$R_1 + R_2 - R_F = 0 \quad (\because R_{F \text{ is open}})$$



$$R_1 + R_2 = 0$$

$$-\frac{V_A}{1} + \frac{3-V_A}{2} = 0$$

$$\frac{1}{1} + \frac{3}{2} = \frac{V_A + V_4}{1} \frac{1}{2}$$


$$\left(\frac{2+3}{2}\right) = \left(\frac{2V_A + V_4}{2}\right)$$

$$5 = 3V_A$$

$$V_A = 5/3 \text{ V}$$

OP-Amp as Differentiator :-

The CKT diagram for Diff.

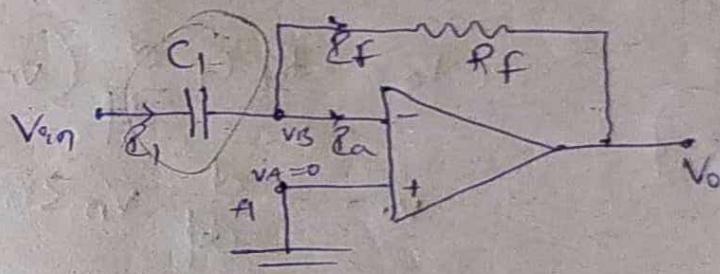

+ calculation of V_O :-

Acc to V.G.C,

$$V_A = V_B = 0$$

⇒ Apply KCL at node B.

$$\sum I_1 - I_2 - I_F = 0$$

$$\sum I_1 - 0 - I_F = 0 \quad (\because I_2 = 0)$$

$$I_1 = I_F \quad \text{--- (1)}$$

⇒ Acc to Ohm's law,

$$I_1 = C_1 \frac{d}{dt} (V_{in} - V_B) \text{ if voltages present.}$$

$$I_1 = C_1 \frac{d}{dt} V_{in} \quad \text{--- (2)}$$

$$R = C \cdot \frac{d V_{in}}{dt}$$

$$\Rightarrow R_f = \frac{V_B - V_o}{R_f} = \frac{0 - V_o}{R_f} = -\frac{V_o}{R_f} \quad \textcircled{3}$$

Sub eq \textcircled{2} \textcircled{3} in eq \textcircled{1}

$$C_1 \frac{d}{dt} V_{in} = -\frac{V_o}{R_f}$$


$$-V_o = R_f C_1 \frac{d}{dt} V_{in}$$

$$V_o = -R_f C_1 \frac{d}{dt} V_{in}$$

$$V_o \propto \frac{d}{dt} (V_{in})$$


Waveforms:
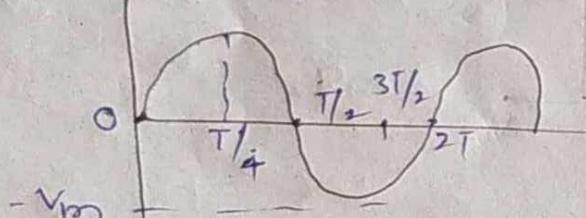
$$V_m \sin \omega t \quad V_{in} = V_m \sin \omega t$$



$$V_o = -R_f C_1 \frac{d}{dt} (V_m \sin \omega t)$$
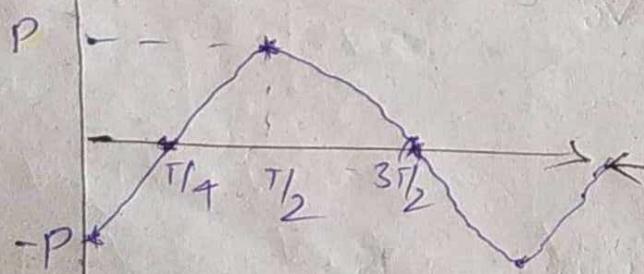
$$V_o = -\frac{d}{dt} V_m \sin \omega t$$




$$V_o = -V_m \cos \omega t \cdot \omega$$

$$= -V_m \omega \cos \omega t$$

$$V_o = -P \cos \omega t$$

$$\left. \begin{cases} t=0 \\ dt+t=T/4 \\ t=T/2 \end{cases} \right\}$$

OP-Amp as Integrator:

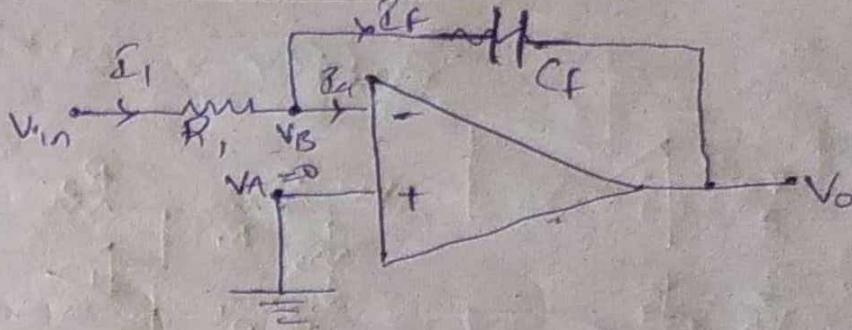

Calc. of V_o :

Acc. to V.G.C,

$$V_A = V_B = 0$$

Acc. to Ohm's law,

$$I_1 = \frac{V_{in} - V_B}{R_1} = \frac{V_{in} - 0}{R_1} = \frac{V_{in}}{R_1}$$

Apply KCL at Node (B):

$$I_1 - I_2 - I_F = 0$$

$$I_1 - 0 - I_F = 0 \quad (\because I_2 = 0)$$

$$I_1 = I_F \quad \text{--- (1)}$$

$$I_F = C_F \frac{d}{dt} (V_B - V_o)$$

$$I_F = C_F \frac{d}{dt} (-V_o)$$

$$I_F = -C_F \frac{d}{dt} (V_o) \quad \text{--- (2)}$$


Sub (1), (2) in (1)

$$\frac{V_{in}}{R_1} = -C_F \frac{d}{dt} (V_o)$$


$$\frac{d}{dt} (V_o) = -\frac{1}{R_1 C_F} V_{in}$$

$$V_o = -\frac{1}{R_1 C_F} \int_0^t V_{in} dt$$

Waveforms:

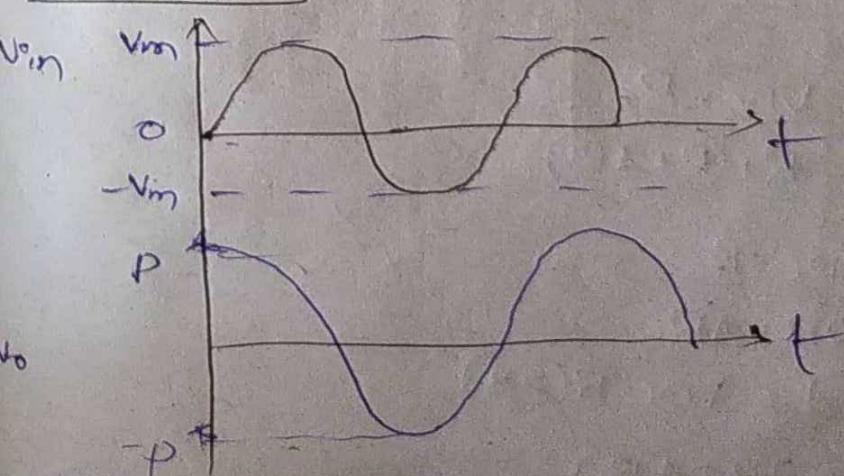


Instrumentation Amplifier

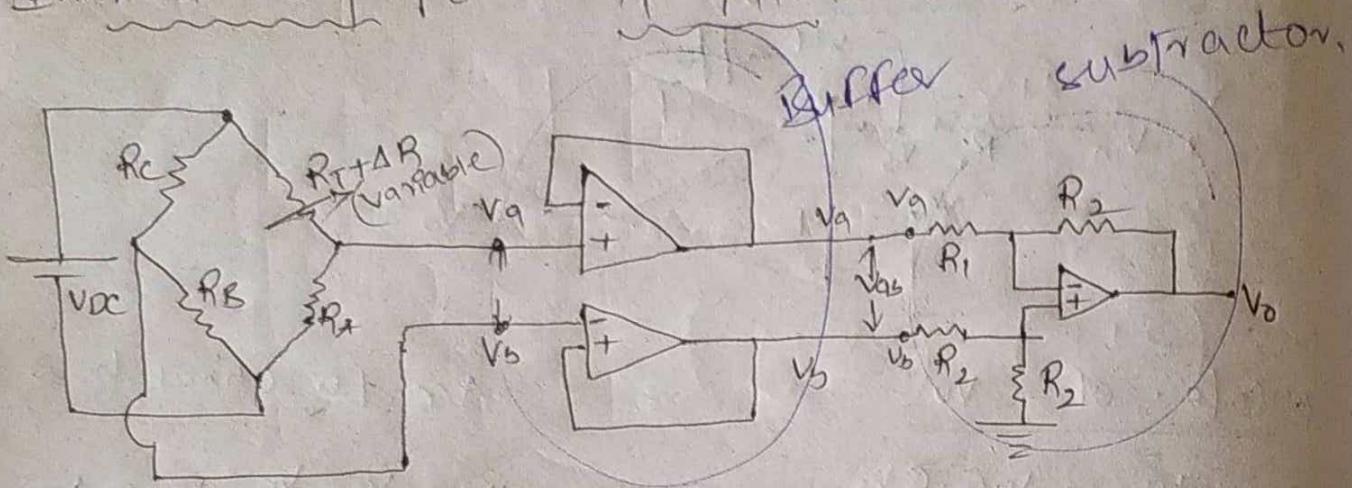

* Calculation of V_O :


Apply NDR,
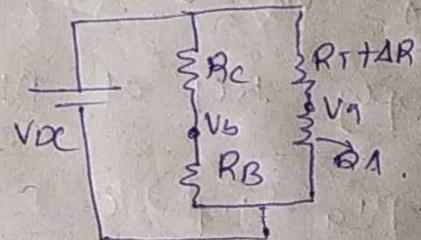
$$V_A = \frac{V_{DC} \cdot R_A}{R_A + (R_T + \Delta R)}$$



$$V_B = \frac{V_{DC} \cdot R_B}{R_B + R_C}$$

* Calc. of V_{AB}

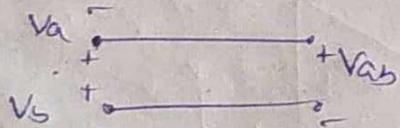

$$-V_B + V_A + V_{AB} = 0$$

$$V_{AB} = V_B - V_A = \frac{V_{DC} \cdot R_B}{R_B + R_C} - \frac{V_{DC} \cdot R_A}{R_A + (R_T + \Delta R)}$$

Assume $R_A = R_B = R_C = R_T = R$.

$$V_{AB} = \frac{V_{DC} \cdot R}{R + R} - \frac{V_{DC} \cdot R}{R + (R + \Delta R)}$$

$$= \frac{V_{DC} \cdot R}{2R} - \frac{V_{DC} \cdot R}{2R + \Delta R}$$

$$= \frac{V_{DC} R (2R + \Delta R) - V_{DC} R (2R)}{2R (2R + \Delta R)}$$

$$\frac{V_{DC} \cdot 2R + V_{DC} \cdot R \Delta R - V_{OC} \cdot R}{2R(2R + \Delta R)}$$

$$V_{ab} = \frac{V_{DC} \cdot \Delta R}{2(2R + \Delta R)}$$

$R \gg \Delta R$

$$V_{ab} = \frac{V_{DC} \cdot \Delta R}{2 \cdot 2R} = \frac{V_{DC} \cdot \Delta R}{4R}$$

The o/p of subtractor is


$$V_o = \frac{R_2}{R_1} (V_b - V_a)$$

$$= A \cdot V_{ab}$$

$$V_o = A \cdot \frac{V_{DC} \cdot \Delta R}{4R}$$

$$\therefore V_o \propto (\Delta R) \quad \text{if } \Delta R = 0 \Rightarrow V_o = 0.$$

* Comparator :

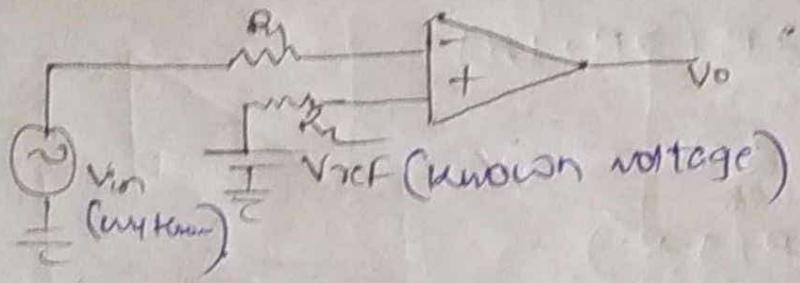

Comparator

Inverting



+ve reference -ve reference

Non-inverting

+ve ref. -ve ref.

* Inverting comparator with +ve Reference :

The ckt diagram shown is

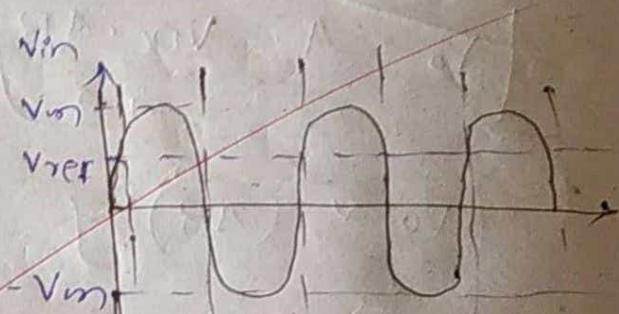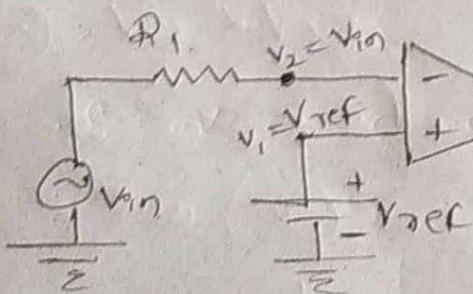

Calculation of V_o :

$$\textcircled{1} \quad V_{in} > V_{ref}$$

$$V_o = -A_d(V_1 - V_2)$$

$$V_1 = V_{in}, \quad V_2 = V_{ref}$$

$$V_o = -A_d(V_{in} - V_{ref})$$

$$= \infty(5 - 3)$$

$$= \infty(+ve)$$

$$V_o = +V_{saturation}$$

$$\textcircled{2} \quad V_{in} < V_{ref}$$


$$V_o = -A_d(V_1 - V_2)$$

$$= -\infty(V_{in} - V_{ref})$$


$$= -\infty(-5 - 3)$$

$$= -\infty(-ve)$$


$$V_o = -V_{sat}$$

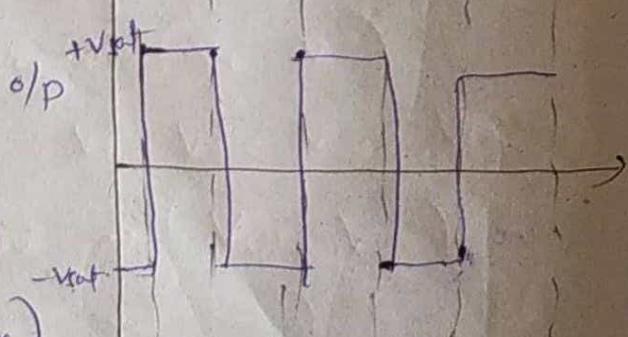

Voltage Transformer curve

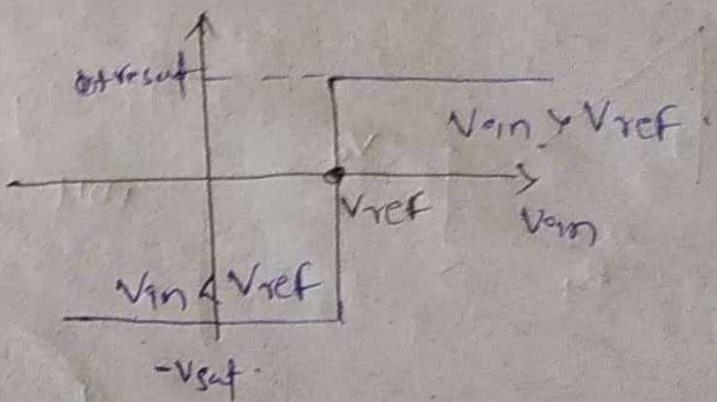

Inverting Comparator with -ve Slope

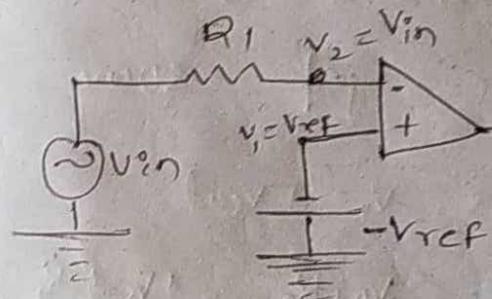


$V_{in} > V_{ref}$

$$V_o = Ad(V_{in} - V_{ref})$$

$$= Ad\left(\frac{V_1 - V_2}{5(-3)}\right), \quad V_1 = V_{in}, \quad V_2 = V_{ref}$$

$$= \infty(+ve)$$

$$V_o = +V_{sat}$$

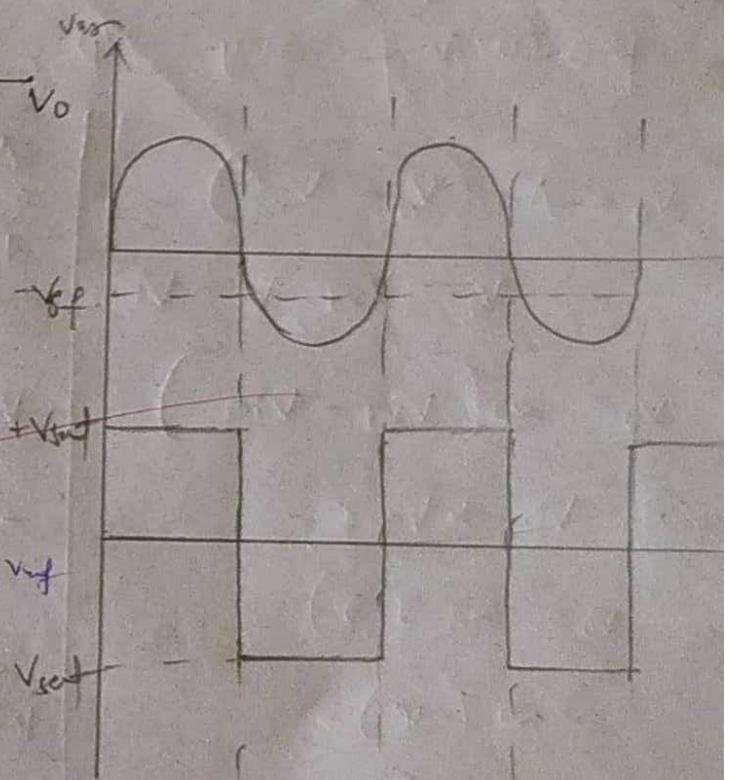

$V_{in} < V_{ref}$

$$V_o = Ad(V_1 - V_2)$$


$$V_o = \infty(V_{in} - V_{ref})$$

$$= \infty(-5 - (-3))$$

$$= \infty(-ve)$$

$$V_o = -V_{sat}$$

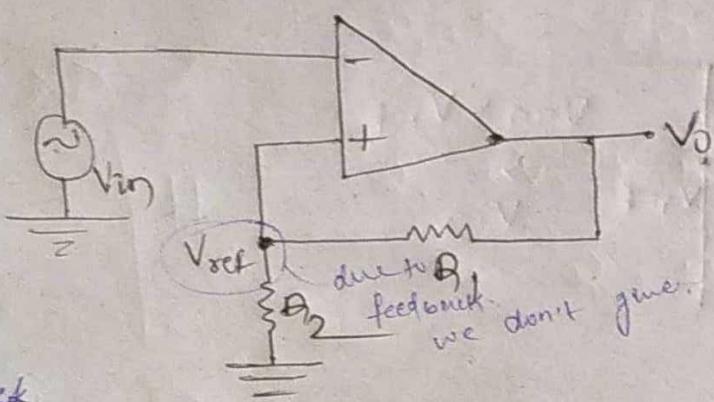* Inverting SCHMITT TRIGGER \div (Regenerative comparator)



* Initially v_o, off set voltages.

* In this we are using +ve feedback.

* Advantage of +ve feedback is without producing any o/p, we get some o/p.

$$V_0 = Ad(V_+ - V_-)$$

$$V_+ = V_{ref}, V_- = V_{in}$$

$$V_0 = \infty(V_{ref} - V_{in})$$

$$\textcircled{1} \quad \frac{V_{in} > V_{ref}}{}$$

$$V_0 = \infty(3-5)$$

$$= \infty(-ve)$$

$V_0 = -V_{sat}$

$$\textcircled{2} \quad \frac{V_{in} < V_{ref}}{}$$

$$V_0 = \infty(3-2)$$

$$= \infty(+ve)$$

$V_0 = +V_{sat}$

$$\text{Assume } V_0 = +V_{sat}$$

$$+V_{ref} = \frac{V_0 \cdot R_2}{R_1 + R_2} = \frac{+V_{sat} R_2}{R_1 + R_2} = V_{UT}$$

upper threshold

$$V_0 = -V_{sat}$$

$$-V_{ref} = \frac{V_0 \cdot R_2}{R_1 + R_2} = \frac{-V_{sat} R_2}{R_1 + R_2} = V_{LT}$$

lower threshold

Working :

$$\textcircled{1} \quad V_{in} < V_{UT}$$

$$V_0 = Ad(V_+ - V_-)$$

$$V_+ = V_{UT}, V_- = V_{in}$$

$$V_0 = \infty(V_{UT} - V_{in})$$

$$= \infty(3-2) = \infty(+ve)$$

$V_0 = +V_{sat}$

$$\textcircled{1} \quad V_{in} > V_{UT}$$

$$V_o = \infty (V_{UT} - V_{in})$$

$$= \infty (3-5)$$

$$= -\infty$$

$$\boxed{V_o = -V_{sat}}$$

$$\textcircled{2} \quad V_{in} > V_{LT}$$

$$V_o = -V_{sat}$$


$$\textcircled{3} \quad V_{in} < V_{LT}$$

$$V_o = \infty (V_{LT} - V_{in})$$


$$= \infty (-3 - (-4))$$

$$\boxed{V_o = +V_{sat}}$$

Waveforms:

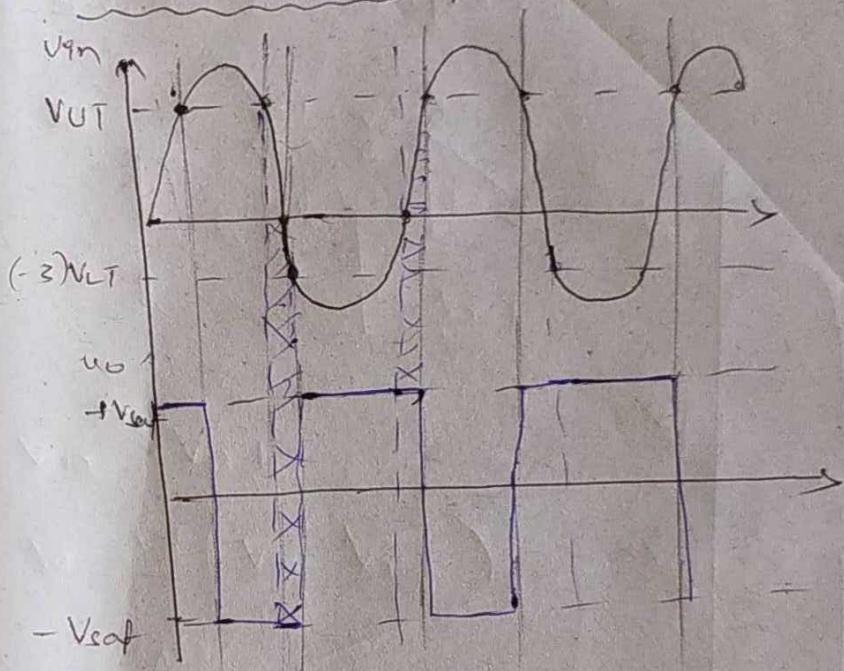

Characteristics:

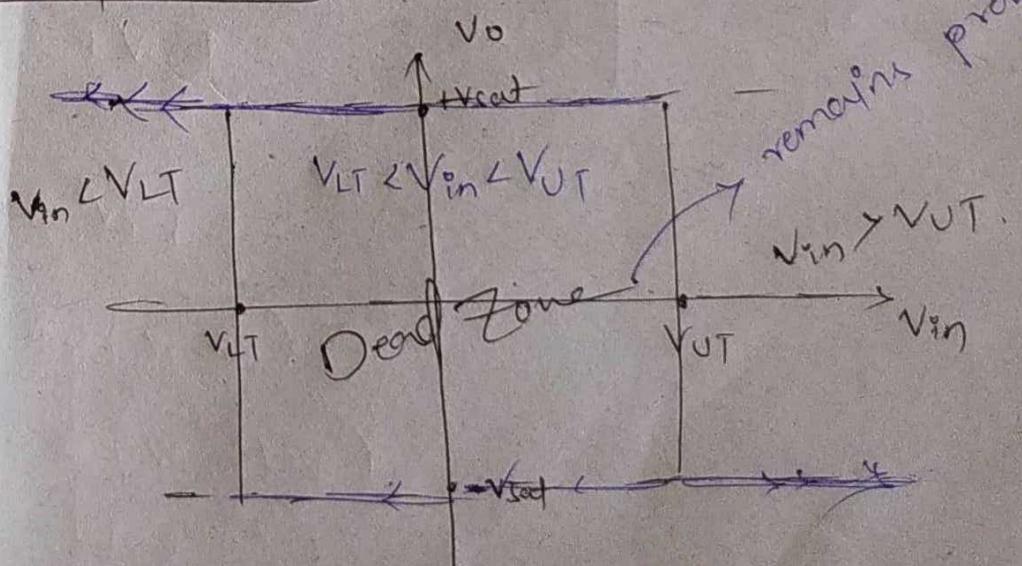

$$\text{Hysteresis } H = V_{UT} - V_{LT}$$

$$= \frac{+V_{sat} \cdot R_2}{R_1 + R_2} - \left(\frac{-V_{sat} \cdot R_2}{R_1 + R_2} \right)$$

$$= \frac{V_{cat} R_1}{R_1 + R_2} + \frac{V_{cat} R_2}{R_1 + R_2}$$

Ans.

$$H = 2 \cdot \frac{V_{cat} R_2}{R_1 + R_2}$$

~~H~~